

## Single Phase AC Circuits

Power is consumed in  $R$  only, but not in  $L$  or  $C$ .

$I_C$  leads  $V_C$  by  $\frac{\pi}{2}$ .

$I_L$  lags  $V_L$  by  $\frac{\pi}{2}$ .

$$P_{avg} = V \cdot I \cos \phi$$

$$\vec{S} = \vec{V} \cdot \vec{I}^* = V \angle 0^\circ \cdot I \angle \phi$$



$$\vec{S} = VI \cos \phi + j VI \sin \phi$$

power  
in VA

$$\vec{S} = P + jQ$$


Active Power  
(W)

Reactive  
Power (VAR)

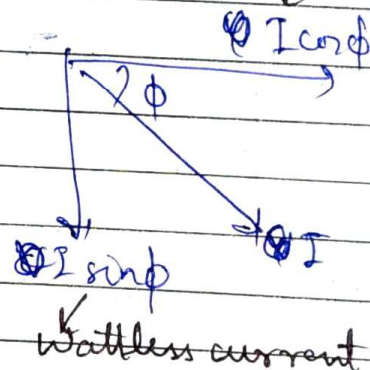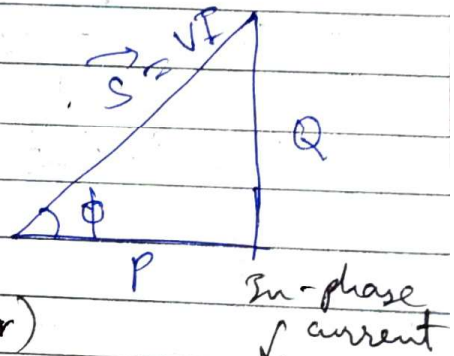


## Series R-L-C Circuits

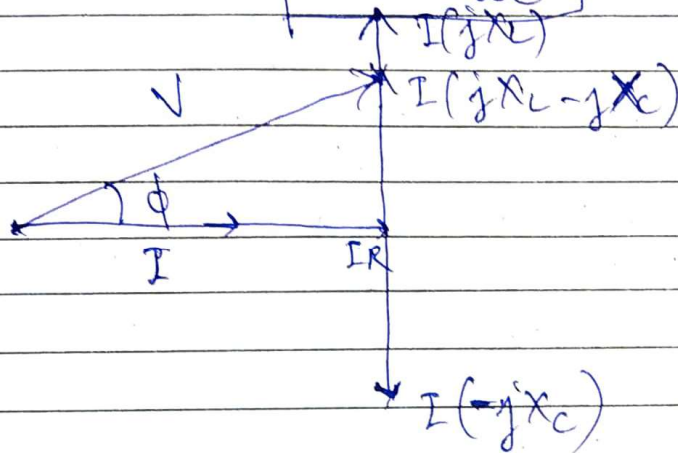(i) Inductive :  $\boxed{\omega L > \frac{1}{\omega C}}$  Current lags vol by  $\phi$ .



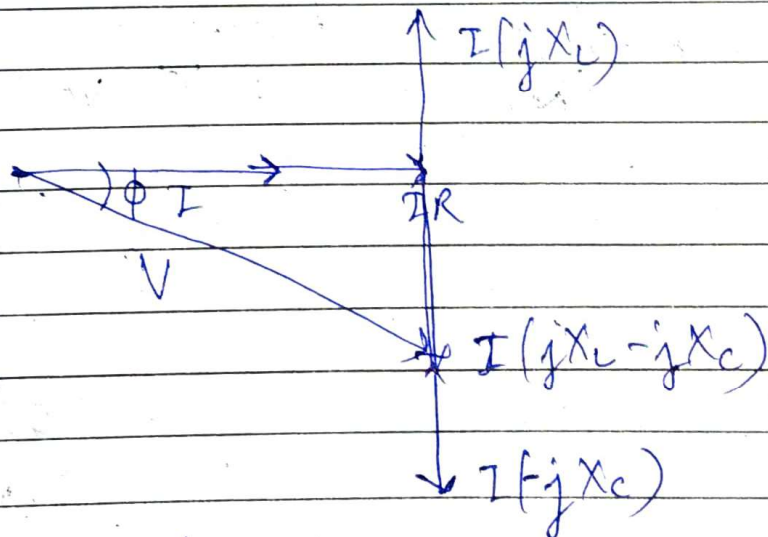(ii) Capacitive :-  $\boxed{\frac{1}{\omega C} > \omega L}$   
Current leads voltage by  $\phi$ .





(iii) Resonance :-  $\boxed{\omega L = \frac{1}{\omega C}}$

$\Rightarrow i \rightarrow \text{max}^m$   
 $\Rightarrow Z \rightarrow \text{min} \& \boxed{Z = R}$  } For Series Resonance

## Parallel R-L-C Circuit

In || circuit, Active Power does not change upon adding a capacitor in parallel.

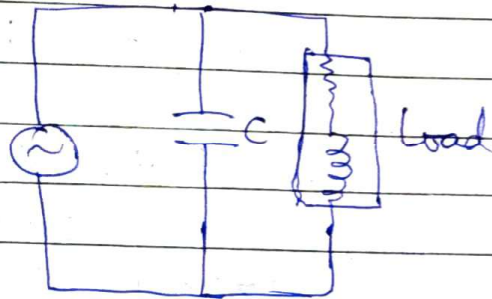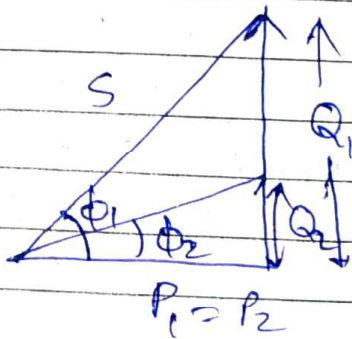

$$Q_C = \Delta Q = Q_1 - Q_2$$

$$= P_1 \tan \phi_1 - P_2 \tan \phi_2$$

$$Q_C = P(\tan \phi_1 - \tan \phi_2) = \frac{V^2}{X_C}$$

### Resonance

Quality Factor =  $\frac{\text{Voltage drop}}{\text{Supply voltage}}$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\text{If } I = \frac{I_m}{\sqrt{2}} \Rightarrow P = \frac{1}{2} I_m^2 R \quad \& \quad Z = \sqrt{2} R$$

The frequencies corresponding to this current are called Half power frequencies.

$$\therefore \text{Band width} = \Delta f = f_2 - f_1 = \frac{R}{2\pi L}$$

$$\text{where } f_1 = f_0 - \frac{\Delta f}{2} \quad \& \quad f_2 = f_0 + \frac{\Delta f}{2}$$



To improve  $Q$  of the coil, it must be designed to have its resistance  $R$  as low as possible. It results in reduction of bandwidth & losses.

### Parallel Resonant Circuits :-

For  $||$  circuits at Resonance, the current  $i$  is minimum &  $Z$  is maximum and

$$|Z| = R$$


$$\phi = 0 \text{ \& } \cos \phi = 1$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \cdot \sqrt{\frac{R_L^2 - 4L/C}{R_C^2 - 4L/C}}$$


bandwidth

At  $f < f_0 \Rightarrow$  Capacitor acts as an open circuit  
 $\Rightarrow$  Net circuit is Inductive

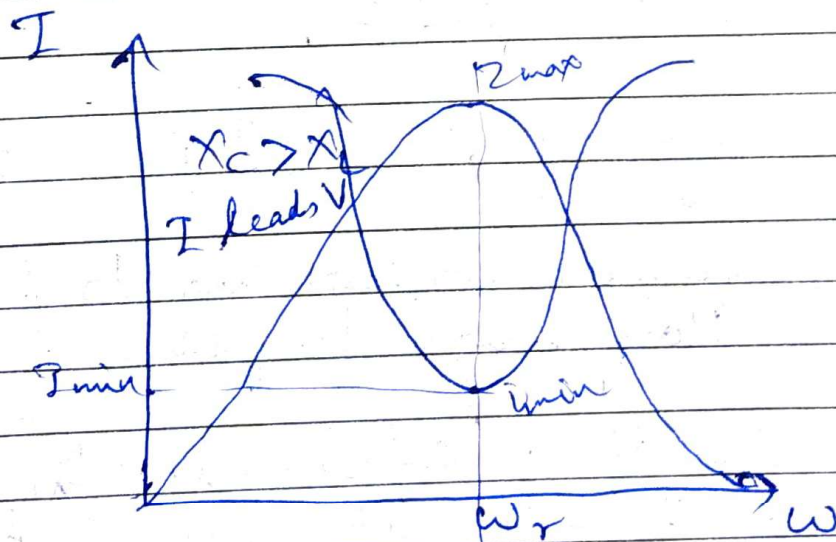At  $f > f_0 \Rightarrow$  Inductor acts as an open circuit  
 $\Rightarrow$  Net circuit is Capacitive



3 $\phi$

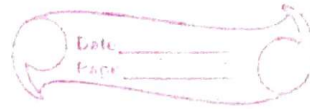


For Star ( $\gamma$ ) connection :-

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

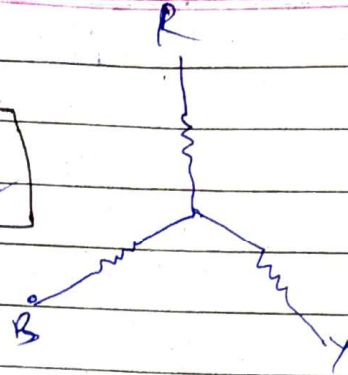
$\Rightarrow V_L$  leads  $V_{ph}$  by  $30^\circ$ .



For Delta Connection :-

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

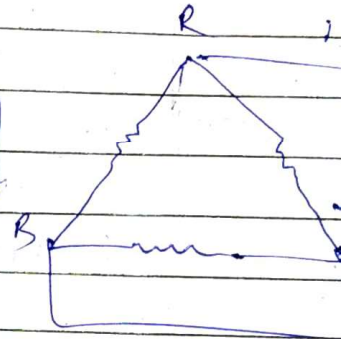

Power in 3 $\phi$  AC :-

Active Power  $P = 3 V_{ph} I_{ph} \cos \phi$  (watts)

Reactive Power  $Q = 3 V_{ph} I_{ph} \sin \phi$  (VAR)

Apparent Power  $S = 3 V_{ph} I_{ph}$  (VA)

For both star & Delta Connection

<u>Star</u>	<u>Delta</u>
$I_L = I_{ph}$	$V_L = V_{ph}$
$V_L = \sqrt{3} V_{ph}$	$I_L = \sqrt{3} I_{ph}$
$P_{ph} = 3 V_{ph} I_{ph} \cos \phi$	$P_{ph} = 3 V_{ph} I_{ph} \cos \phi$
$P_{line} = \sqrt{3} \times \frac{V_L}{\sqrt{3}} \times I_L \cos \phi$	$P_{line} = \sqrt{3} \times \frac{I_L}{\sqrt{3}} \cos \phi$
$P_{line} = \sqrt{3} V_L I_L \cos \phi$	$P_{line} = \sqrt{3} V_L I_L \cos \phi$



$$P = \sqrt{3} V_L I_L \cos \phi \text{ (watt)}$$

$$Q = \sqrt{3} V_L I_L \sin \phi \text{ (VAR)}$$

$$S = \sqrt{3} V_L I_L \text{ (V.A)}$$

For Both  
Star & Delta  
Connection.

### Numericals

Assume all quantities ( $V, I, P$ ) to be line quantities until & unless they are specified as phase quantities (for both star & delta).

$Z$  is always in terms of phase.

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

If  $V_{ph}$  &  $Z_{ph}$  are given then calculate first  $I_{ph}$

After that,  $I_L = \sqrt{3} I_{ph}$  (Delta)

→ For phasor, we need  $V_m, I_m$  &  $\phi$  for  $I_L = I_{ph}$  (star)

$$V_m = \sqrt{2} V_{rms} = \sqrt{2} V_L$$

$$I_m = \sqrt{2} I_L$$

For star connected lagging P.f load :-

$$P = W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

$$W_1 - W_2 = V_L I_L \sin \phi$$

$$\tan \phi = \sqrt{3} \left[ \frac{W_1 - W_2}{W_1 + W_2} \right]$$

$$\phi = \tan^{-1} \left[ \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right]$$

$$\cos \phi = \checkmark$$