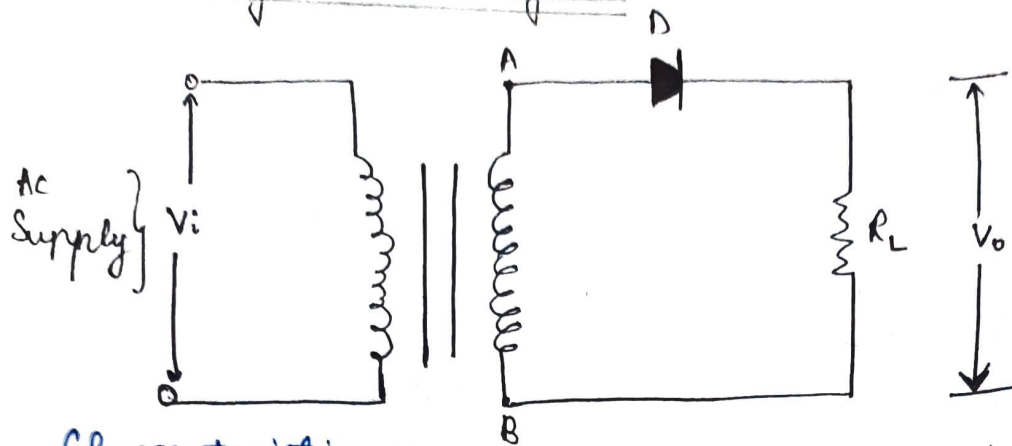


Electronics Assignment

Riya Jaiswal
200106058



Ans 1) Half Wave Rectifier




Characteristics :-

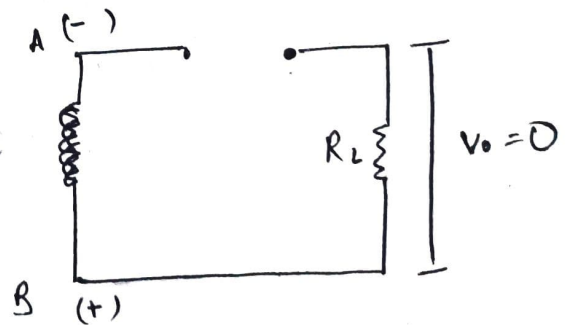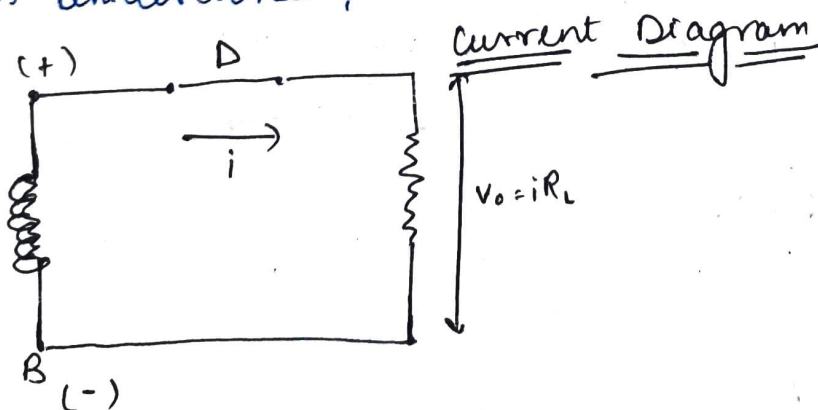- i) In half wave rectifier, single diode is used
- ii) It gives output only in one cycle.
- iii) Step-down transformer is used.

Working :- During the first half cycle of AC input, when terminal A of secondary is suppose positive and B is negative. The diode is forward biased, hence it conducts and current flows through load. During the second half cycle of AC input the terminal A is negative and B is positive. The diode is now reverse biased. Hence there is almost zero current and zero output voltage across R_L . The process is repeated. Thus the output current is unidirectional, but intermittent and ~~pulsating~~ pulsating.



waveform :-

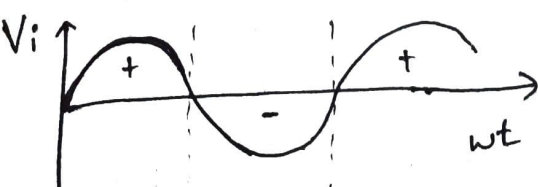

Ripple factors:-

$$RF = \frac{\text{rms value of ac component of O/P}}{\text{dc value}}$$

$$V_{rms}^2 = V_{(ac)rms}^2 + V_{dc}^2$$

$$V_{(ac)rms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$\therefore RF = \frac{V_{dc} \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}}{V_{dc}}$$

$$R.F = \sqrt{(F.F)^2 - 1}$$

(F.F - form factor)

$$F.F = \frac{V_{rms}}{V_{avg}} = \frac{V_{m/2}}{V_m/\pi} = \frac{\pi}{2} = 1.57$$

$$R.F = \sqrt{(1.57)^2 - 1}$$

$$R.F = 1.21 \quad (\underline{\text{Ans}})$$

* Efficiency:- $\eta\% = \frac{\text{O/P DC power}}{\text{I/P AC power}} \times 100\%$

$$= \frac{I_{dc}^2 R}{I_{rms}^2 R} \times 100\%$$

$$\left\{ \begin{array}{l} I_{dc} = I_m/\pi \\ I_{rms} = I_m/2 \end{array} \right\}$$

$$= \frac{4}{\pi^2} \times 100\%$$

$$\eta\% = 40.56\%$$

* % Regulation

$$\% = \frac{V_{dc} (\text{no load}) - V_{dc} (\text{full load})}{V_{dc} (\text{full load})} \times 100\%$$

$$V_{dc} (\text{no load}) = V_m / \pi$$

$$V_{dc} (\text{full load}) = I_{dc} \times R_L = \frac{I_m}{\pi} \times R_L$$

$$= \frac{V_m R_L}{\pi (R_L + R_s + R_f)}$$

$$\left\{ I_m = \frac{V_m}{R_L + R_s + R_f} \right\}$$

On putting these values in equation


$$\% \text{ regulation} = \frac{\frac{V_m}{\pi} - \frac{V_m R_L}{\pi (R_s + R_L + R_f)}}{\frac{V_m R_L}{\pi (R_L + R_s + R_f)}} \times 100\%$$

On solving,

$$= \frac{R_L + R_s + R_f - R_L}{R_L} \times 100\%$$

$$\therefore \% \text{ Regulation} = \frac{R_s + R_f}{R_L} \times 100\%$$

FULL WAVE RECTIFIER

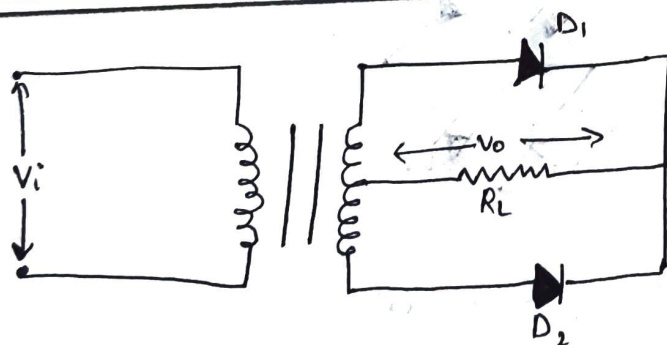



Characteristics :-

- Two diodes are used in full wave centre tapped rectifier
- Secondary winding of transformer is centre tapped for using TUF (Transformer utilisation factor)



Working - During positive half cycle diode D_1 become forward biased and act as short circuit and diode D_2 become reverse bias and act as open circuit. Diode D_1 conduct the current through R_L

and gives O/P.

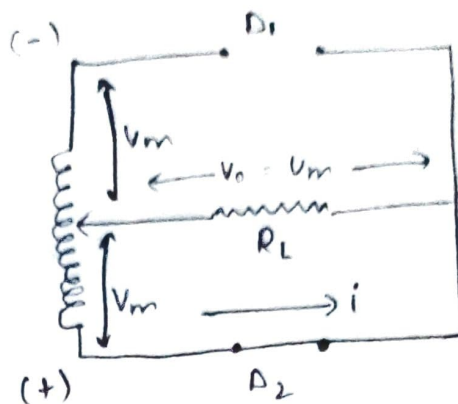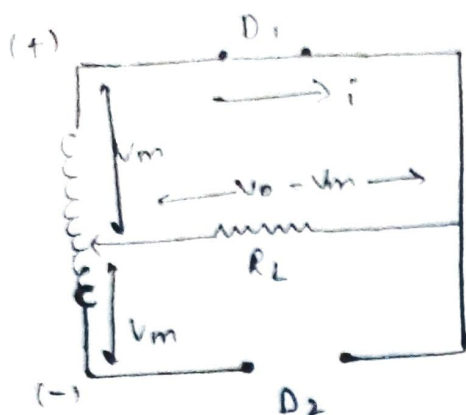
During the negative half cycle, diode D_1 become reverse bias and act as open circuit and diode D_2 become forward bias and act as short circuit diode D_2 conducts the current through load resistance R_L and gives output.



* Waveform

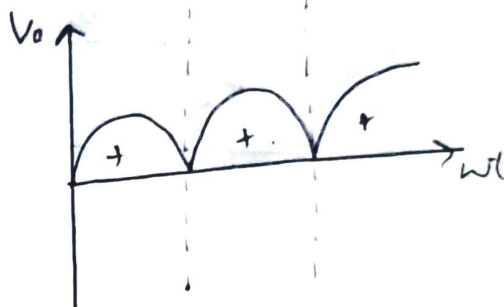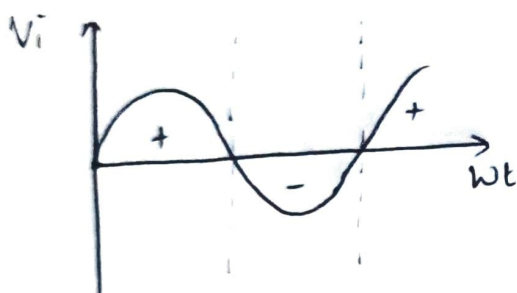

* Bridge Rectifier

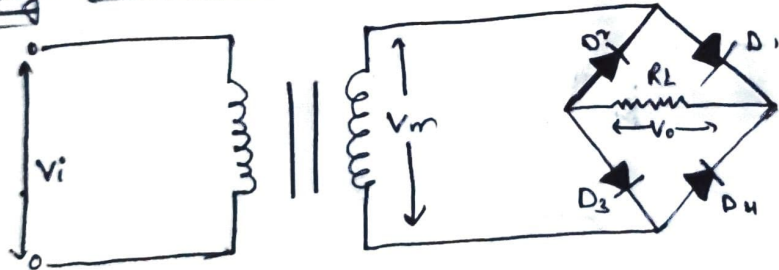


Characteristics :-

- * Four diodes are used in bridge rectifier.
- * Bridge rectifier offers full wave rectification.
- * Bridge combination of diode is connected with secondary winding of transformer.


Working :- During positive half cycle, diode D_1 and D_3 become forward bias and D_2 , D_4 become reverse bias. Diode D_1 and D_3 act as short circuit and passes the current through R_L . Diode D_2 and D_4 act as open circuit and do not conduct the current.

During the negative half cycle, D_1 and D_4 act as forward bias and D_2 and D_3 become reverse bias. Diode D_2 and D_4 conduct the current through R_L .

(+)

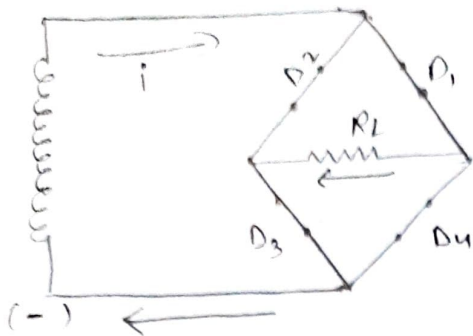

(-)

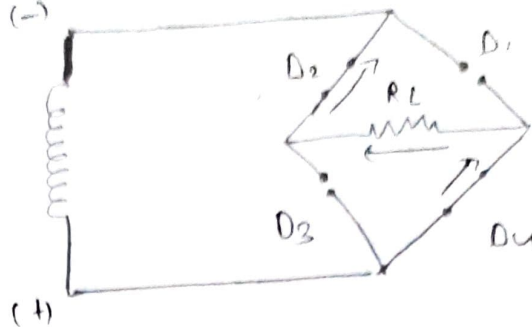

* Ripple factor

$$R.F = \sqrt{(F.F)^2 - 1}$$

$$F.F = \frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{2}}{2 V_m/\pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$R.F = \sqrt{(1.11)^2 - 1} \Rightarrow \boxed{R.F = 0.48}$$

* Efficiency

$$\eta \% = \frac{O/P \text{ DC power}}{I/P \text{ AC power}} \times 100\%$$

$$= \frac{I_{dc}^2 R}{I_{rms}^2 R} \times 100\% = \frac{4 I_m^2 / \pi^2}{I_m^2 / 2} \times 100\%$$

$$= \frac{8}{\pi^2} \times 100\%$$

$$\begin{cases} I_{dc} = 2I_m/\pi \\ I_{rms} = I_m/\sqrt{2} \end{cases}$$

$$\eta \% = 81.13\%$$

* % regulation:-

$$\% \text{ regulation} = \frac{V_{dc}(\text{no load}) - V_{dc}(\text{full load})}{V_{dc}(\text{full load})} \times 100\%$$

$$V_{dc}(\text{no load}) = 2 \frac{V_m}{\pi}$$

$$V_{dc}(\text{full load}) = \frac{2V_m}{\pi} \cdot \frac{R_L}{R_s + R_L + R_f}$$

$$\% \text{ regulation} = \frac{\frac{2V_m}{\pi} - \frac{2V_m}{\pi} \left\{ \frac{R_L}{R_L + R_s + R_f} \right\}}{\frac{2V_m}{\pi} \cdot \frac{R_L}{R_L + R_s + R_f}}$$

$$= \frac{\frac{2V_m}{\pi} \left\{ 1 - \frac{R_L}{R_s + R_L + R_f} \right\}}{\frac{2V_m}{\pi} \cdot \frac{R_L}{R_L + R_s + R_f}}$$

$$\% \text{ regulation} = \frac{R_s + R_f}{R_L} \times 100\%$$

* Comparative study of half wave, centre tap and bridge rectifier :-

	Half wave	Centre-tap	Bridge
<u>Ripple factor</u>	1.21	0.48	0.48
<u>Efficiency</u>	40.6%	81.13%	81.13%
<u>% regulation</u>	0%	0%	0%