

14/12/2020

## MODULE - 1

### DC Circuit Analysis and Network Theorems

#### \* Sources



- Ideal sources
- Practical sources

Sources can also be classified as:-

- Voltage sources
- Current sources

#### → Voltage sources

- Ideal Voltage sources

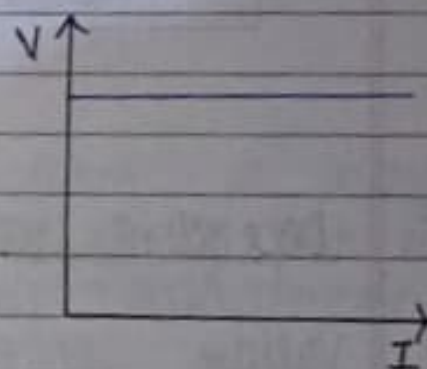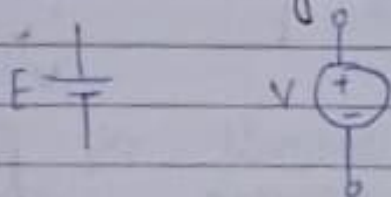


Voltage across the ideal voltage source remains constant irrespective of current.

- Practical Voltage sources





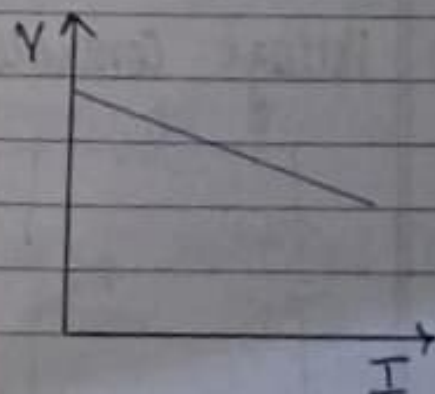When  $I \uparrow$  then  
 $V_{ab} \downarrow$ .




## • Current Source


### • Ideal current source

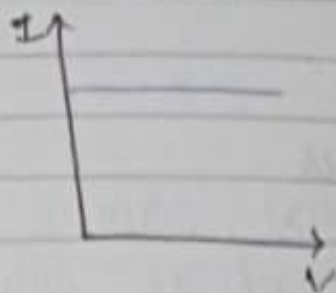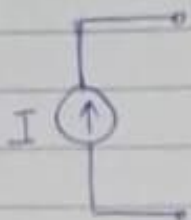


### • Practical current source

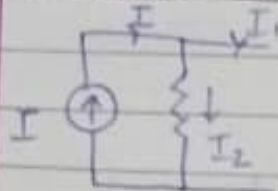

$$I_1 < I$$

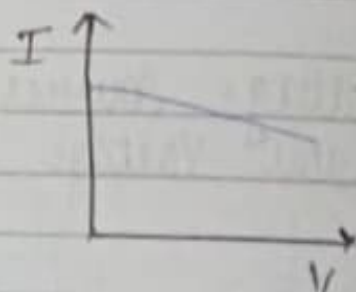

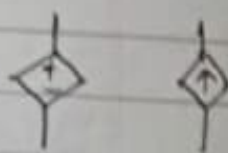
## \* Dependent voltage / current source (Also called controlled source)




- Voltage controlled voltage source (VCVS)
- Current controlled voltage source (CCVS)
- Voltage controlled current source (VCCS)
- Current controlled current source (CCCS)
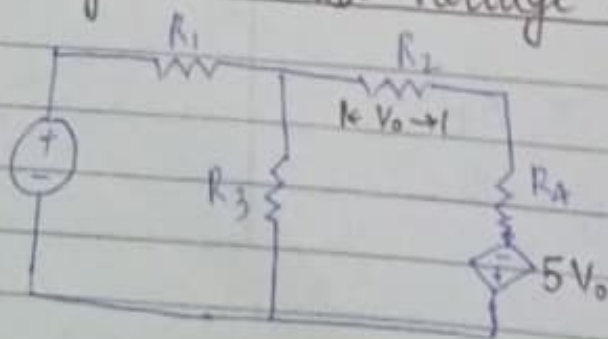
### i) Voltage Controlled Voltage Source (VCVS) -



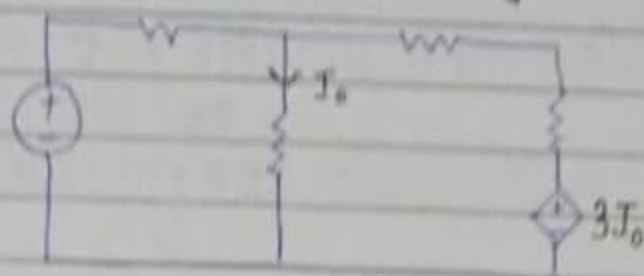ii) Current Controlled Voltage Source (CCVS) -



\* Unilateral / Bilateral Elements

If an element changes its characteristic on changing the direction of current passing through it, it is an unilateral element.  
Eg - pn junction, transistor

If the element does not change its characteristics on changing the direction of current passing through it, it is a bilateral element.  
Eg - Resistors, Inductors

\* Active / Passive Elements

If any element has internal energy source to drive the ckt, then it is an active element.

Eg - Voltage source, semiconductor devices.

If any element does not have internal energy source to drive the ckt, then it is a passive element.

Eg - R, L, C



## \* Linearity

- Homogeneity
- Superposition

### i) Homogeneity

$$f(ax) = a f(x)$$

Eg:  $f(x) = 7x$

$$\begin{aligned} f(ax) &= 7(ax) \\ &= a(7x) \\ &= a f(x) \end{aligned}$$

$$\begin{aligned} f(x) &= 3x^2 \\ f(ax) &= 3(ax)^2 \\ &= 3a^2x^2 \\ &= a^2 f(x) \\ f(ax) &\neq a f(x) \end{aligned}$$

It is also called scaling property.

### ii) Superposition

It is also called additive property.


$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

$$\begin{aligned} f(x) &= 7x \\ f(x_1 + x_2) &= 7(x_1 + x_2) \\ &= 7x_1 + 7x_2 \\ &= f(x_1) + f(x_2) \end{aligned}$$


$$\begin{aligned} f(x) &= 3x^2 \\ f(x_1 + x_2) &= 3(x_1 + x_2)^2 \\ &= 3x_1^2 + 3x_2^2 + 6x_1x_2 \\ f(x_1 + x_2) &\neq f(x_1) + f(x_2) \end{aligned}$$

## \* R, L and C as linear elements

R:  $V = IR$

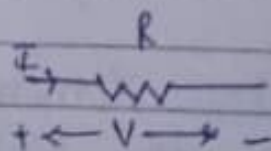

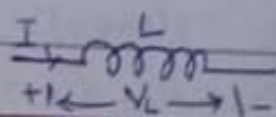L:  $V_L = L \frac{dI}{dt}$  (Non-linear)




$I = \frac{1}{L} \int V dt$

$$\boxed{\phi = LI} \quad (\text{linear})$$


$$C \therefore I = C \frac{dV_c}{dt}$$

$$V_c = \frac{1}{C} \int I dt$$


$$\boxed{Q = CV}$$

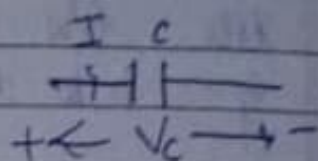

### \* Source Transformation

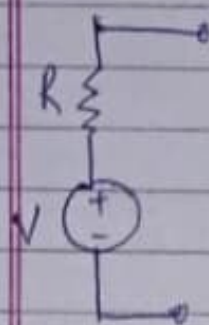


$$V = IR$$

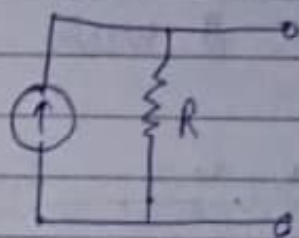
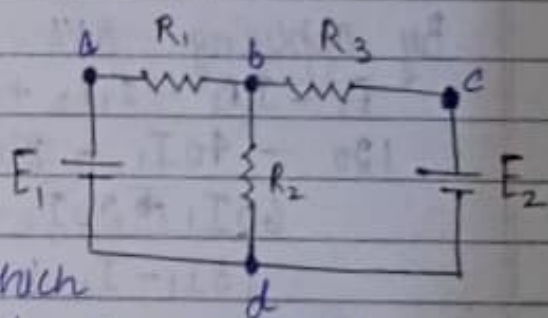
### \* Loop Analysis

Node - A node of a circuit is an equipotential point at which 2 or more components are connected.  
Eg- a, b, c, d / elements



Junction A junction of a circuit is an equipotential point at which 3 or more elements are connected.  
Eg- b, d

Branch - It is that part of the ckt. which lies b/w 2 junction.


Eg - b to d, (c), b to d(1), b to d(2)

Loop - Any closed path in a ckt is a loop.

Eg - 3 loops.

Mesh - The individual / elementary loops are called mesh.

Eg - 2 mesh

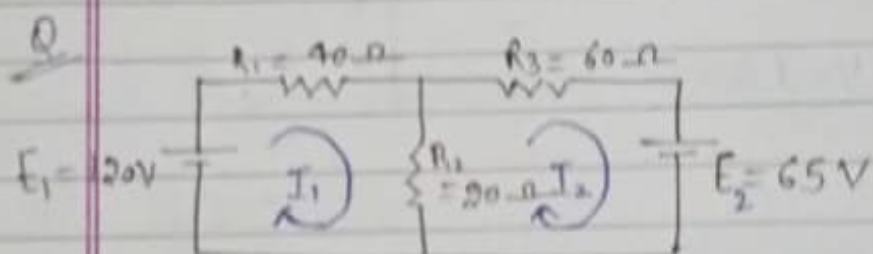

By applying KVL in Loop 1

$$E_1 - I_1 R_1 - I_1 R_2 + I_2 R_2 = 0$$

$$120 - 40I_1 - 20I_1 + 20I_2 = 0$$

$$60I_1 - 20I_2 = 120$$

$$3I_1 - I_2 = 6 \quad \text{--- (1)}$$

By applying KVL in Loop 2

$$-E_2 - I_2 R_2 + I_1 R_2 - I_2 R_3 = 0$$

$$-65 - 20I_2 + 20I_1 - 60I_2 = 0$$

$$20I_1 - 80I_2 = 65$$

$$4I_1 - 16I_2 = 13 \quad \text{--- (2)}$$

Solving (1) & (2)



$$48 I_1 - 16 I_2 = 96$$

$$4 I_1 - 16 I_2 = 13$$

$$44 I_1 = 83$$


$$I_1 = \frac{83}{44} \text{ Amp.}$$

$$I_2 = \frac{63 \times 83 - 6}{44}$$

$$= \frac{249 - 264}{44}$$

$$= -\frac{25}{44}$$
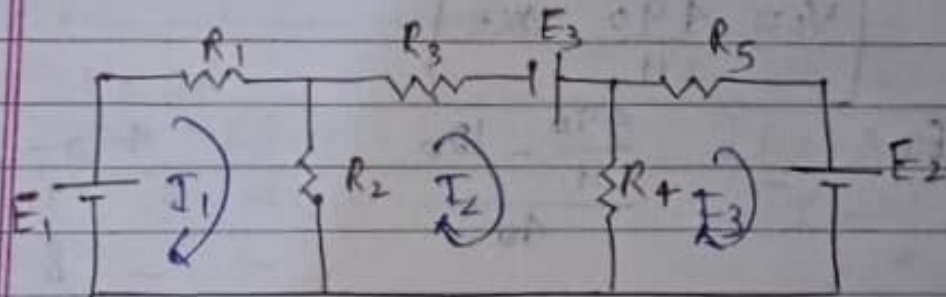
$$I_2 = \frac{25}{44} \text{ Amp. (In opp. direction we assumed)}$$



In loop 1 :-

$$E_1 - I_1 R_1 - I_1 R_2 + I_2 R_2 = 0 \quad \text{--- (1)}$$

In loop 2 :-

$$E_3 - I_2 R_4 + I_3 R_4 - I_2 R_2 - I_2 R_3 = 0 \quad \text{--- (2)}$$


In loop 3 :-

$$-E_2 - I_3 R_4 + I_2 R_4 - I_3 R_5 = 0 \quad \text{--- (3)}$$

# \* Nodal Analysis :-

Applying KCL,

$$I_1 + I_2 + I_3 = 0$$

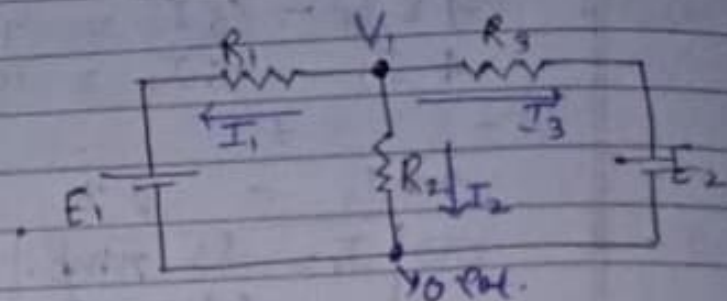

$$\frac{V_1 - E_1}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - E_2}{R_3} = 0$$

$$E_1 = 120V, \quad E_2 = 65V$$

$$R_1 = 40\Omega, \quad R_2 = 20\Omega, \quad R_3 = 60\Omega$$

$$\frac{V_1 - 120}{40} + \frac{V_1}{20} + \frac{V_1 - 65}{60} = 0$$

$$\frac{3V_1 - 360}{120} + \frac{6V_1}{120} + \frac{2V_1 - 130}{60} = 0$$

$$11V_1 = 490$$


$$V_1 = \frac{490}{11} \text{ Volt}$$

$$I_1 = \frac{V_1 - E_1}{R_1} = \frac{\frac{490}{11} - 120}{40} = \frac{490 - 1320}{11 \times 40} = -\frac{830}{440} = -\frac{83}{44} \text{ amp}$$

$$I_2 = \frac{V_1}{R_2} = \frac{\frac{490}{11}}{20} = \frac{49}{22} \text{ amp}$$
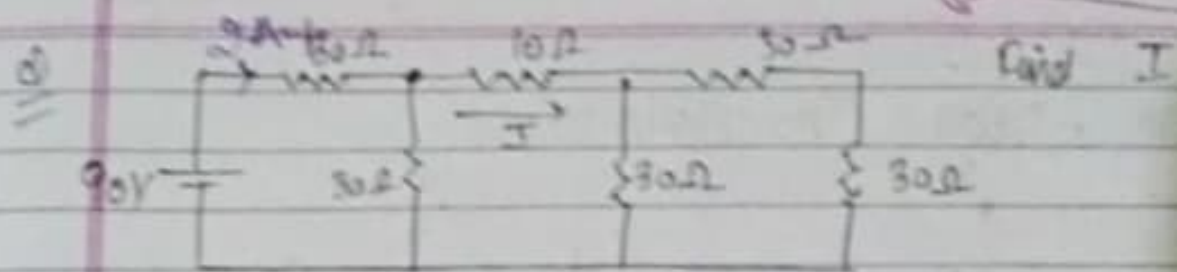
$$I_3 = \frac{\frac{490}{11} - 65}{60} = \frac{490 - 715}{60 \times 11} = -\frac{225}{660} = -\frac{15}{44} \text{ amp}$$






$$\frac{1}{R} = \frac{1}{30} + \frac{1}{60} = \frac{2}{60} \Rightarrow R = 30 \Omega$$

$$\text{Total } R = 45 \Omega$$

$$V = IR$$

$$I' = 90/45 = 2 \text{ Amp}$$
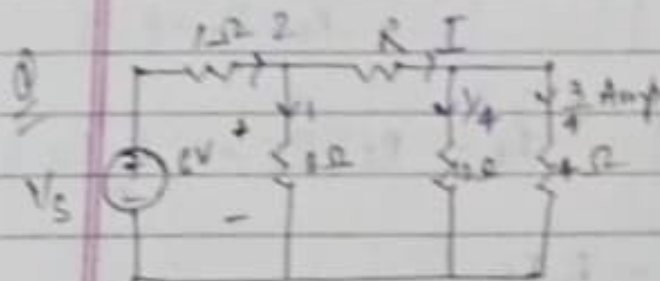
$$I = \frac{I'}{2} = \frac{2}{2} = 1 \text{ amp}$$



Find i)  $R$  &  $V_s$

ii) Power output of source  $V_s$ .

$$V = IR$$

$$6 = 1(R + 3)$$

$$R = 3 \Omega$$

$$\frac{1}{R_p} = \frac{1}{1\Omega} + \frac{1}{4\Omega} \quad \left| \quad 12 \times I' = 4 \times \frac{3}{4} \right.$$

$$R_p = 3 \Omega \quad \left| \quad I = \frac{1}{4} \right.$$

$$I = \frac{1}{4} + \frac{3}{4} = 1 \text{ A}$$

$$V_s = IR$$

$$= 2 \times 4$$



$$V_s = 8 \text{ Volt}$$

$$\text{ii) Power} = V_s \times I$$

$$= 8 \times 2$$

$$P = 16 \text{ watt}$$

# \* Star - Delta Transformation

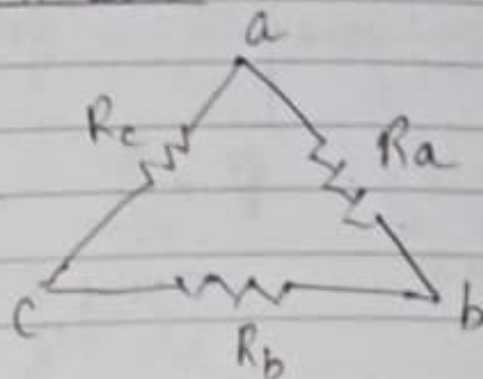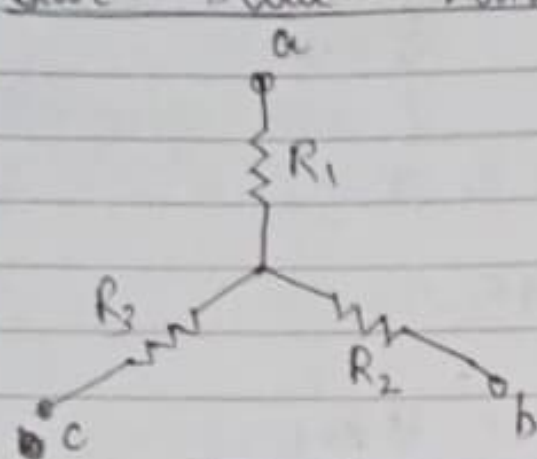

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_a = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_b = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_c = R_3 + R_1 + \frac{R_1 R_3}{R_2}$$