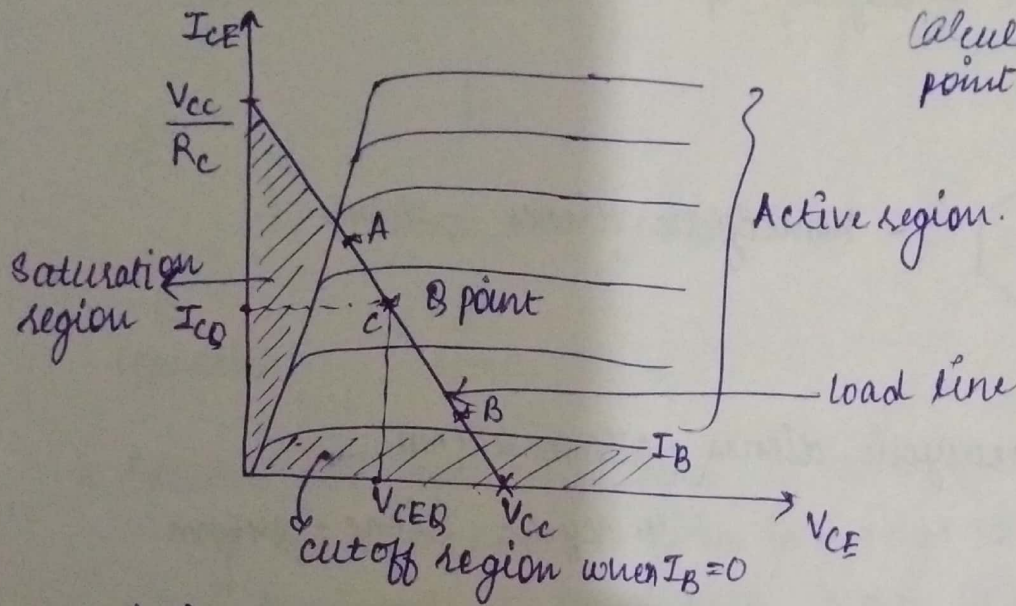


DC biasing - BJT:

→ Selection of Operating Point (selected on load line)

Calculation of operating point \equiv value of V_{CE} and I_C



Active Region:

EB \rightarrow FB (forward bias)
CB \rightarrow Reverse bias

- * When operating point is selected near saturation point the current signal gets clipped in the +ve half and the voltage signal gets clipped in the -ve half.
- * When the operating point is selected near cutoff region current signal gets clipped in -ve part and voltage signal clipped in positive part
- * Operating point must be selected at the middle of load line.
- * When collector current varies operating point changes.

for common base confi $I_C = \beta I_B + (\beta + 1) I_{CBO}$ $\rightarrow I_{CBO} \equiv$ Reverse leakage current

10°C Rise in temp

$I_{CBO} \Rightarrow$ Double

$$I_C = \beta I_B + I_{CEO}$$

common emitter config.

→ Stability Factor:

rate of change of collector current w.r.t. I_{CBO} at constant V_{BE} & β .


$$S = \left. \frac{dI_C}{dI_{CBO}} \right|_{\text{const. } V_{BE} \text{ \& } \beta}$$

$$s' = \frac{dI_C}{dV_{BE}} \Big|_{\text{const. } I_{CBO} \& \beta}$$

$$s'' = \frac{dI_C}{d\beta} \Big|_{\text{const. } I_{CBO} \& V_{BE}}$$


Lower the value of S , stabler the system.

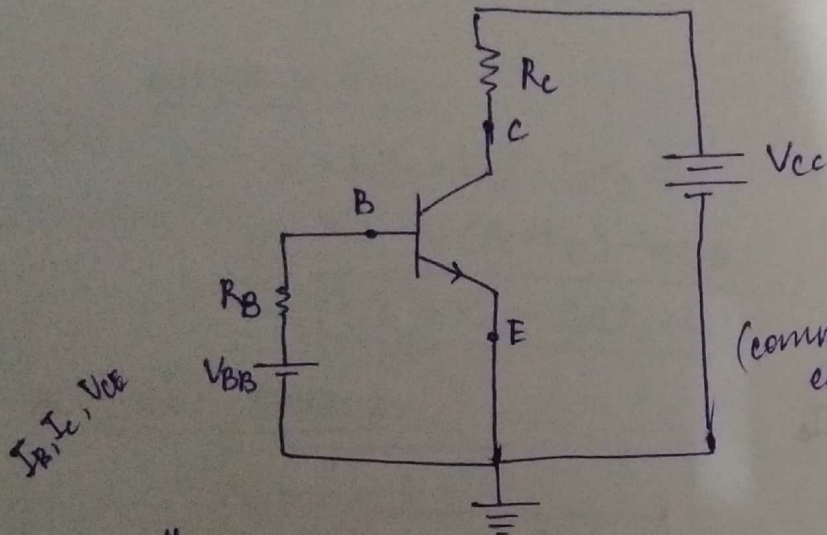→ Fixed Bias circuit: / Base Bias circuit



R_B is selected in such a way so as to make V_{BE} equal to
 $0.7V \xrightarrow{\text{for}} \text{silicon.}$
 $0.3V \xrightarrow{\text{for}} \text{Germanium}$

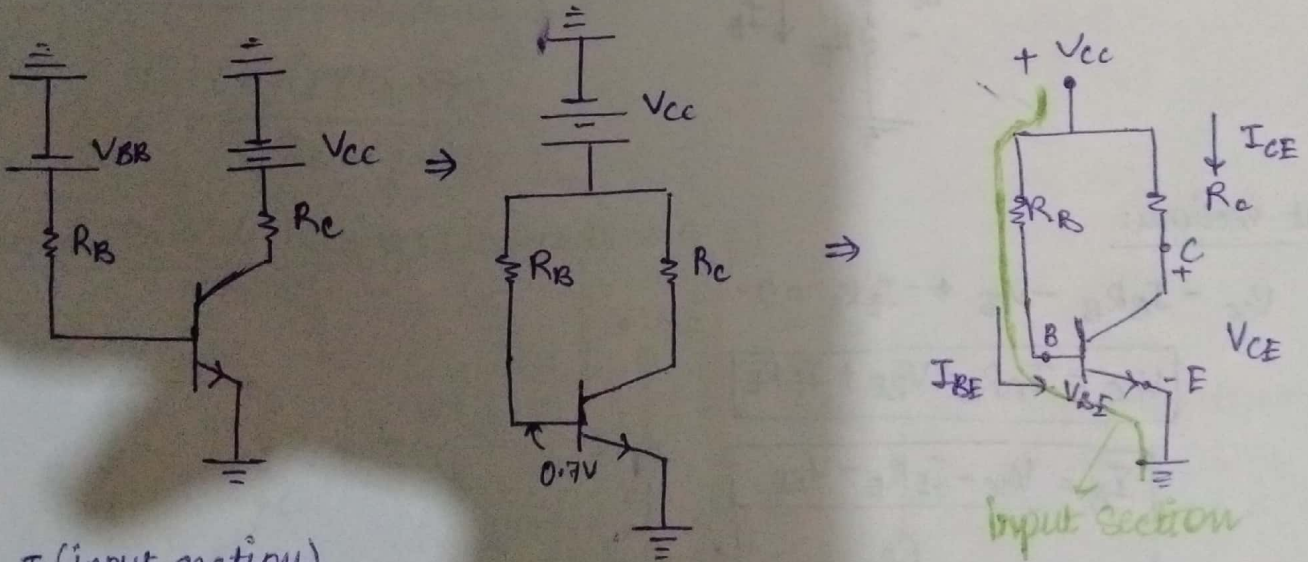↓ since 2 batteries are not practically applied thus we modify it.



I (input section)

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B \approx \frac{V_{CC}}{R_B}$$

$$I_C = \beta I_B + I_{CBO}$$

$$I_C \approx \beta I_B$$

$$I_C \approx \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

Output section:

$$+V_{CC} - I_E R_E - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


→ Stability factor : (Fixed Bias Circuit)

$$S = \beta + 1$$

general equation that can be used for any system

$$S = \frac{\beta + 1}{1 - \beta \frac{dI_B}{dI_C}}$$

→ Emitter Bias circuit:

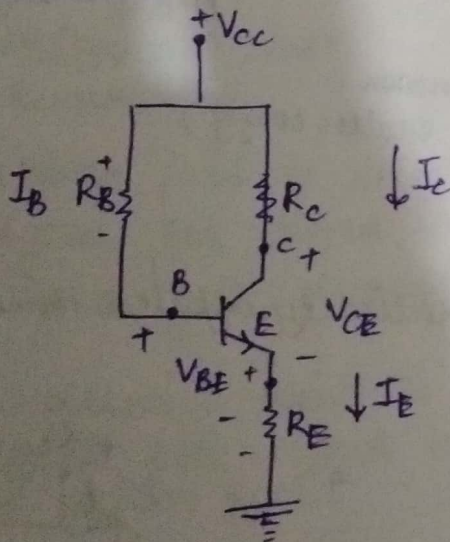

input section:

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$I_B = \frac{V_{CC} - I_E R_E - V_{BE}}{R_B}$$

⊗ $T \uparrow \Rightarrow I_{CBO} \uparrow \Rightarrow I_{CEO} \uparrow \Rightarrow I_C \uparrow \rightarrow I_E \uparrow \Rightarrow I_E R_E \uparrow \Rightarrow I_B \downarrow \Rightarrow I_C \downarrow$
 $\Rightarrow I_C \uparrow \text{ and } \downarrow$

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$V_{CC} - I_B [R_B + (\beta + 1) R_E] - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \beta \left[\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \right]$$

$$I_E = I_B + I_C$$

$$I_E = (\beta + 1) I_B$$

output section:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$


$I_C \approx I_E$
as I_B is in μA .

* Stability factor:


$$S = \frac{\beta + 1}{1 + \beta \left(\frac{R_E}{R_B + R_E} \right)}$$

$$S = \frac{(\beta + 1) (R_B + R_E)}{R_B + (\beta + 1) R_E}$$


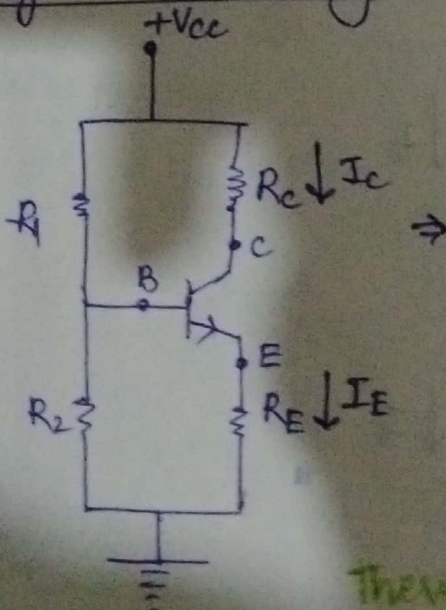
→ Voltage Divider Biasing: (independent of β)



Theremin part


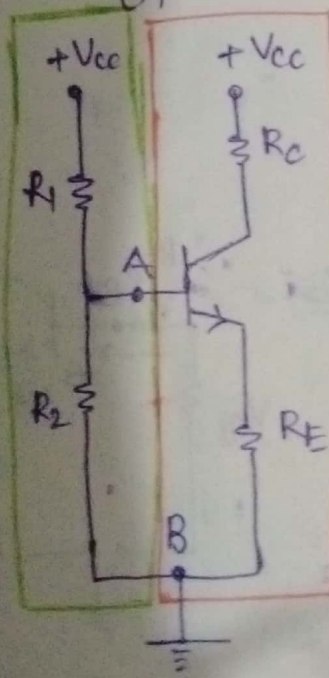


Theremin theorem used.

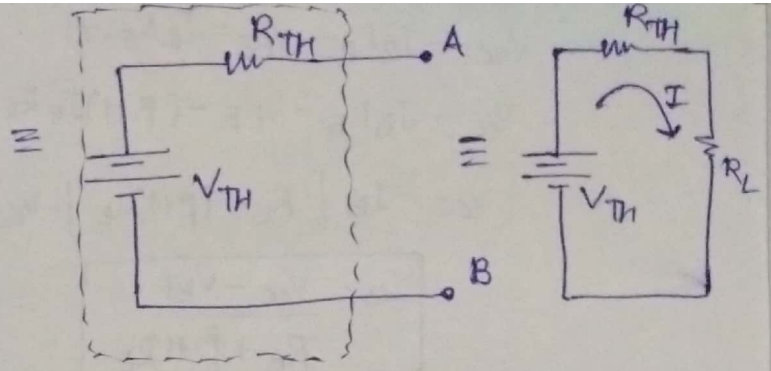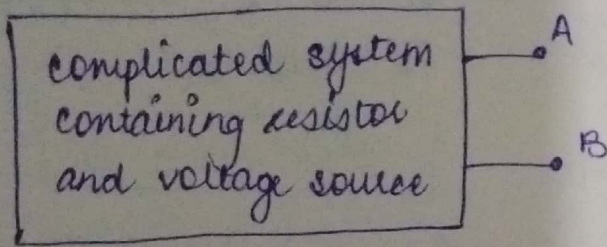

V_{TH} = Thevenin voltage across A, B

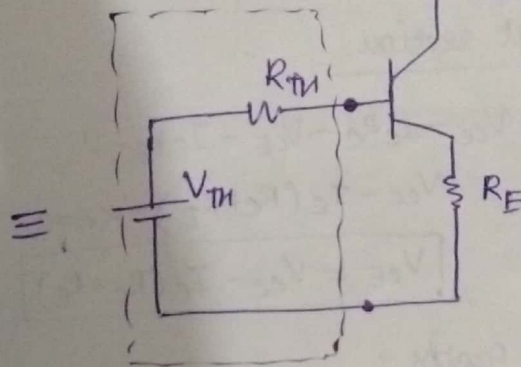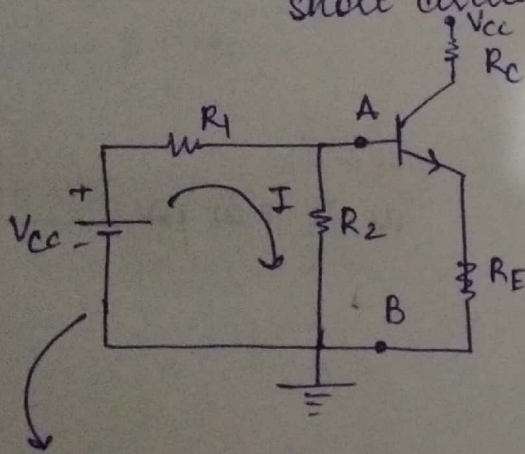R_{TH} = Resistance when all voltage source are short circuited.





current $I = \frac{V_{CC}}{R_1 + R_2}$



$V_{TH} = R_2 \times I$

$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$

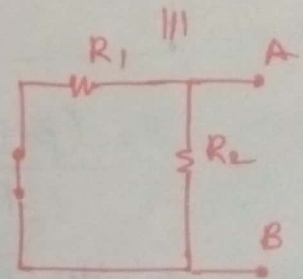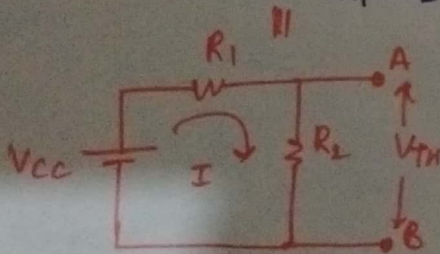$V_{TH} = \frac{R_2 \times V_{CC}}{R_1 + R_2}$



now,

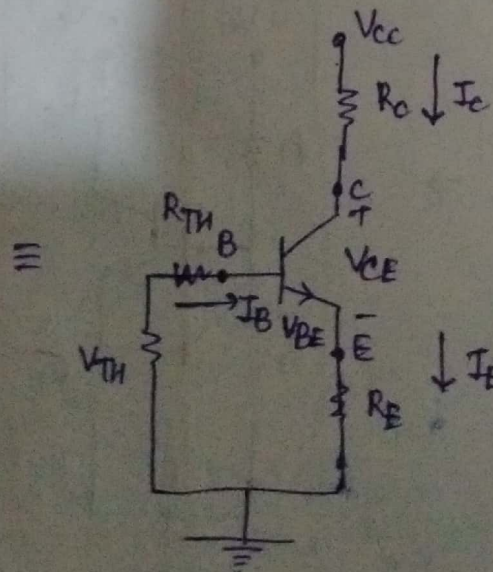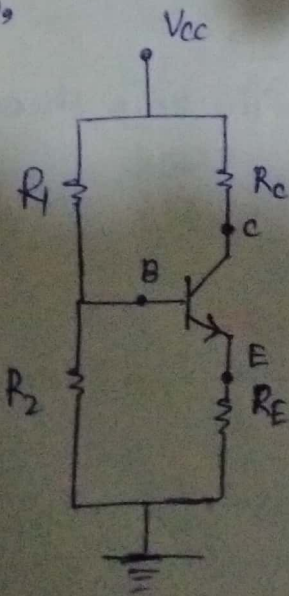

Input section:

$$V_{TH} - R_{TH} I_B - V_{BE} - I_E R_E = 0.$$

$$V_{TH} - R_{TH} I_B - V_{BE} - (\beta + 1) I_B R_E = 0.$$

$$V_{TH} - I_B (R_{TH} + (\beta + 1) R_E) - V_{BE} = 0.$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

$$I_C = \beta \left[\frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E} \right]$$

output section:

$$I_E \approx I_C.$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0.$$

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0.$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

now, $I_C = \beta \left[\frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E} \right]$

$$I_C \approx \beta \left[\frac{V_{TH} - V_{BE}}{R_{TH} + \beta R_E} \right]$$


when $R_{TH} \ll \beta R_E$

$$I_C \approx \beta \left[\frac{V_{TH} - V_{BE}}{\beta R_E} \right]$$

Stability Factor:

$$S = \frac{\beta + 1}{1 + \beta \frac{R_E}{R_{TH} + R_E}}$$

→ Collector Feedback Configuration:

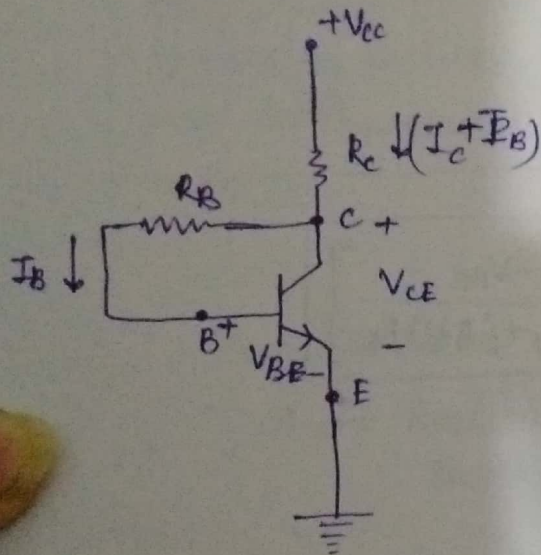

Input section:

$$V_{CC} - R_C(I_C + I_B) - I_B R_B - V_{BE} = 0.$$

$$V_{CC} - I_B(R_C + R_B) - I_C R_C - V_{BE} = 0.$$

$$I_B = \frac{V_{CC} - V_{BE} - I_C R_C}{R_C + R_B} \quad \text{--- (3)}$$

$$I_C = \beta \left[\frac{V_{CC} - V_{BE} - I_C R_C}{R_C + R_B} \right] \quad \text{--- (1)}$$

Output section

$$V_{CC} - R_C(I_C + I_B) - V_{CE} = 0. \quad (\because I_B \ll I_C)$$

$$V_{CC} - R_C I_C - V_{CE} = 0.$$

$$V_{CE} = V_{CC} - I_C R_C \quad \text{--- (2)}$$

put eq (2) in (1) & (3).

$$I_B = \frac{V_{CE} - V_{BE}}{R_C + R_B}$$

$$I_C = \beta \frac{V_{CE} - V_{BE}}{R_C + R_B}$$

$\uparrow \Rightarrow I_{CBO} \uparrow \Rightarrow I_C \uparrow \Rightarrow V_{CE} \downarrow \Rightarrow I_B \downarrow \Rightarrow I_C \downarrow$
 $\Rightarrow I_C \uparrow \& \downarrow$ simultaneously. Hence provides stability.


$$V_{CC} - I_B(R_C + R_B) - I_C R_C - V_{BE} = 0.$$

$$V_{CC} - I_B(R_C + R_B) - \beta I_B R_C - V_{BE} = 0.$$

$$V_{CC} - I_B((\beta + 1)R_C + R_B) - V_{BE} = 0.$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_C + R_B}$$

→ Emitter-Follower Configuration:

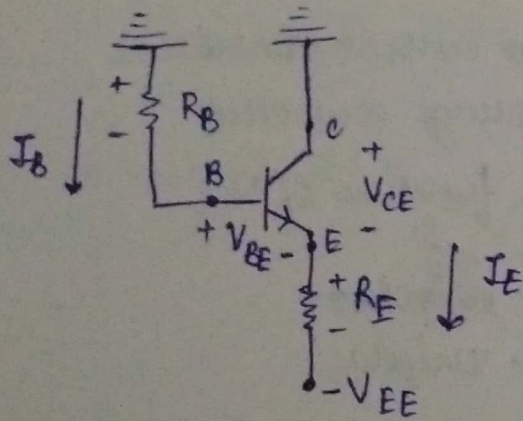

Input section:

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$-I_B R_B - V_{BE} - (\beta + 1) I_B R_E + V_{EE} = 0$$

$$-I_B (R_B + (\beta + 1) R_E) - V_{BE} + V_{EE} = 0$$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1) R_E}$$


$$I_E = \beta I_B$$

Output section:

$$-V_{CE} - I_E R_E + V_{EE} = 0$$

$$V_{CE} = V_{EE} - I_E R_E$$

Field Effect Transistor:

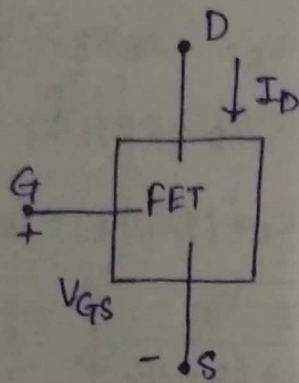

BJT \rightarrow ~~co~~ current controlled


FET \rightarrow voltage controlled.

I_D is a function of V_{GS}

BJT \rightarrow ~~non~~ bipolar


FET \rightarrow unipolar

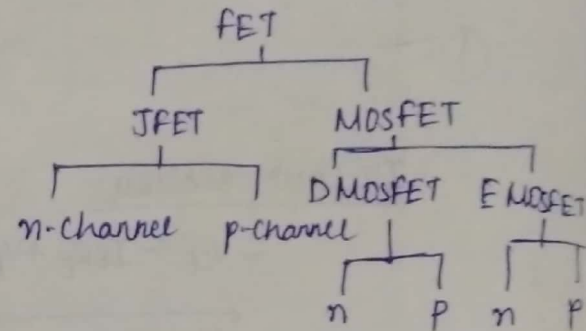\rightarrow FET for amplification & switching.



- \rightarrow FET have high input impedance
- more temp. stable
 - smaller in size
 - less sensitive for input signals.

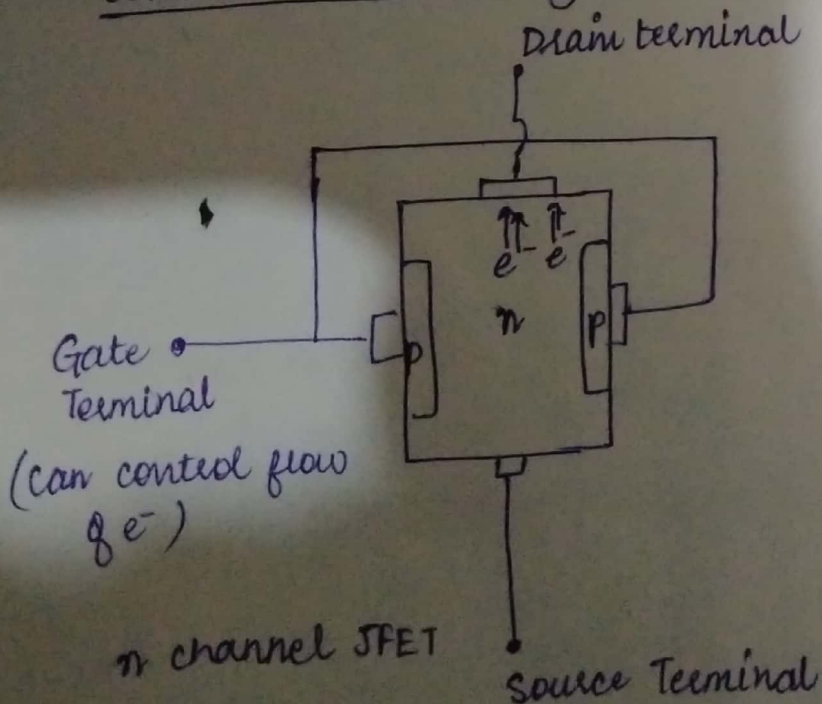\rightarrow construction & working of JFET:




JFET \rightarrow has 2 p-n junctions.

\downarrow
2 depletion region


cause of e^- flow = voltage diff. b/w D & S.

when $V_{GS} = 0 \Rightarrow$ voltage of G and S are same and $V_{DS} > 0V$
 e^- goes in drain


n channel JFET

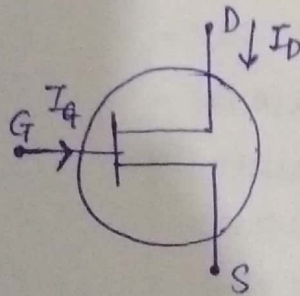

p channel

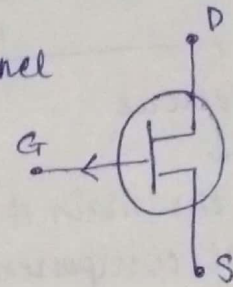

pinch off voltage:

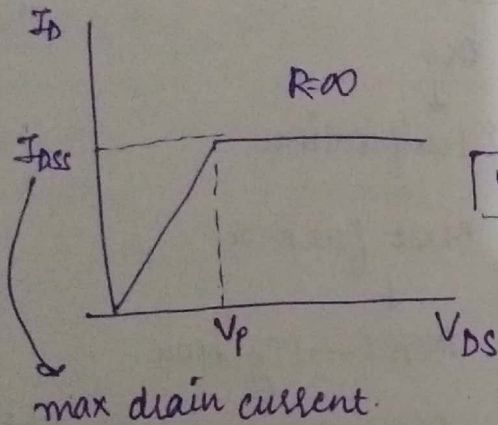

$$V_{GS} = 0, (V_D > |V_P|)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$





$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

$$P_D = V_{DS} I_D$$

$$I_D = I_S, I_G \approx 0A$$

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

MOSFET:

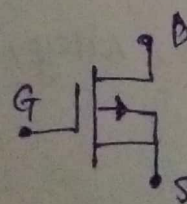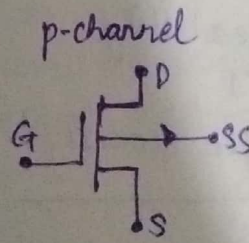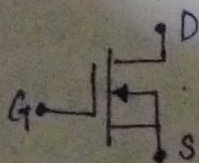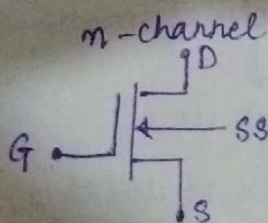

$$V_T = V \text{ at which } I_D \approx 0A$$

$$V_{DG} = V_{DS} - V_{GS}$$

$$V_{DS(\text{sat})} = V_{GS} - V_T$$

$$I_D = K(V_{GS} - V_T)^2$$