


## DC CIRCUIT ANALYSIS:-

- ① Active Elements - which supply energy to Network. Eg - Voltage source
- ② Passive Elements - which dissipate or store Energy. Eg - capacitor, Inductor, Resistor
- ③ Unilateral Elements - whose properties depend upon the direction of current. Eg. - Diode, Transistor.
- ④ Bilateral Elements - whose properties doesn't depend upon the direction of current. Eg. - Resistance, Inductor, Capacitor



⇒ Active and Passive Network -

- ★ A Network is said to be passive if it contains no source of emf in it.
- ★ When a network contains one or more sources of emf or current then it's said to be active.


⑤ Ideal and Practical voltage source -

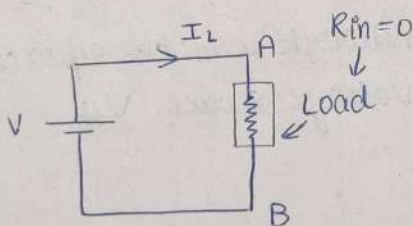

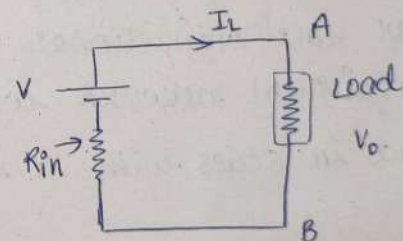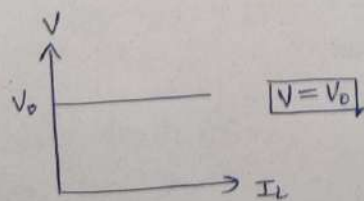⇒ The source which maintains a constant voltage across the load, irrespective of the load current.




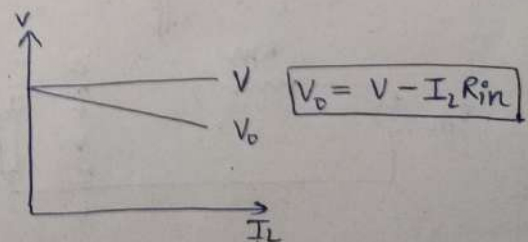⇒ The source whose output terminal voltage decreases as we increase the load resistance.






## ⑥ Ideal and Practical current source.

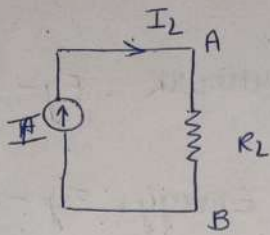

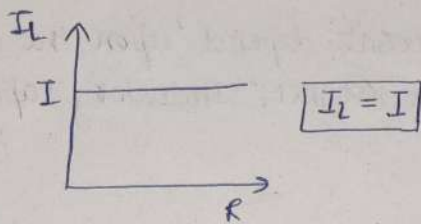⇒ The source which delivers constant current to the load irrespective of load resistances.






★ Internal Resistance of Ideal source is  $\infty$ .


## Source Transformation
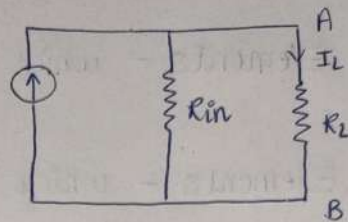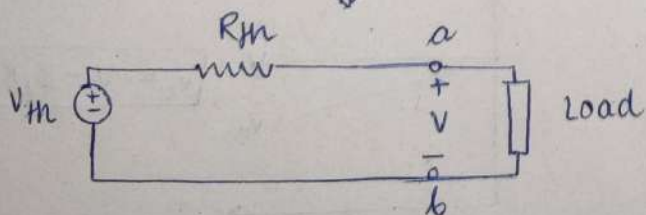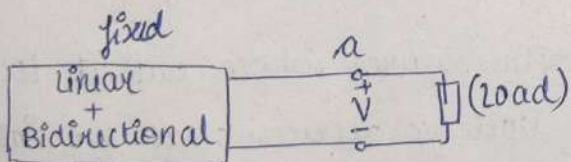
### THEVENIN'S THEOREM :-

A linear and bidirectional two-terminal network can be replaced by an equivalent network consisting of a voltage source  $V_{th}$  connected in series with a resistor  $R_{th}$ .



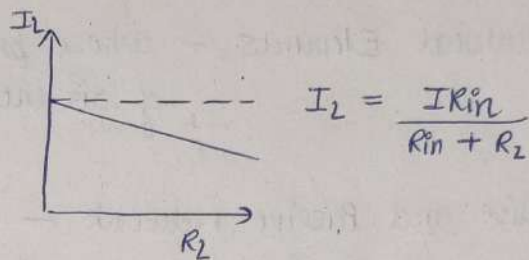
⇒ The source whose output current decreases as we increase the load resistance.



## Nodal Analysis

- ① Assign voltage at every node and one node is taken as reference. (with Pot. = 0V)
- ② Develop KCL Eq. and solve.

### Sample Problem -:

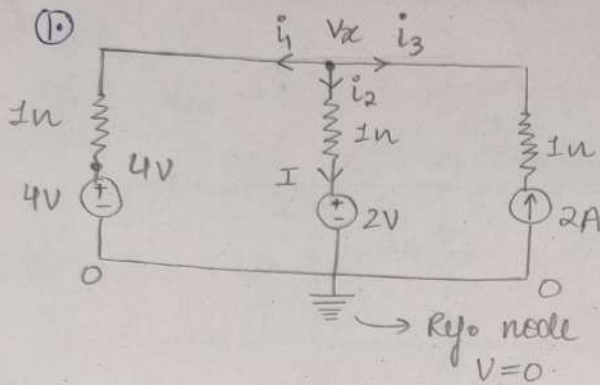

opp the net current so (-)

$$V_x - iR - V = V_y$$


$$i = \frac{V_x - V_y - V}{R}$$

$$I_1 + I_2 + I_3 = 0$$

$$I_3 = -2A$$

$$\frac{(V_x - 0) - 4}{1} + \frac{(V_x - 0) - 2}{1} + \frac{-2}{1} = 0$$

$$V_x = 4V$$

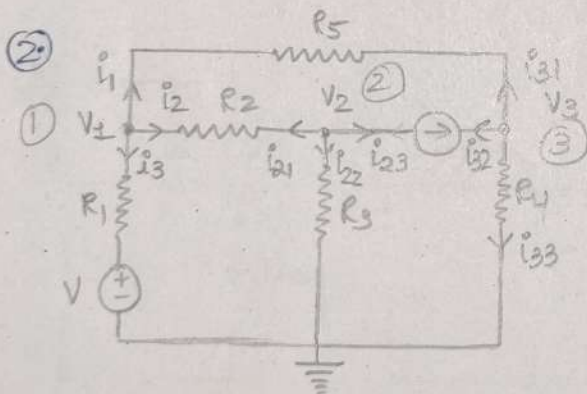

considering Node ① -:

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 - V_3}{R_5} + \frac{(V_1 - V_2)}{R_2} + \frac{(V_1 - V)}{R_1} = 0$$

considering Node ③ -:

$$i_{31} + i_{32} + i_{33} = 0$$

$$\frac{(V_3 - V_1)}{R_5} + \frac{V_3 - V_2}{R_4} (-I) + \frac{(V_3 - 0)}{R_4} = 0$$

considering Node ② -:


$$i_{21} + i_{22} + i_{23} = 0$$

$$\frac{(V_2 - V_1)}{R_2} + \frac{V_2}{R_3} + I = 0$$



# Sample Problem Thevenin's Theorem :-


①

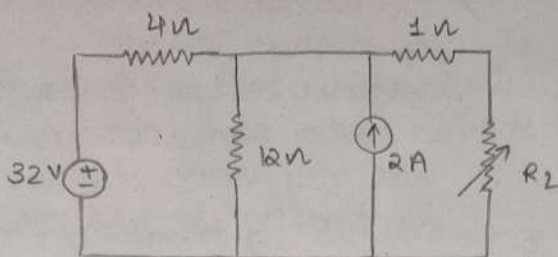

Find  $V_{th}$  and  $R_{th}$  for the circuit.

②

$V_{th}$  :-

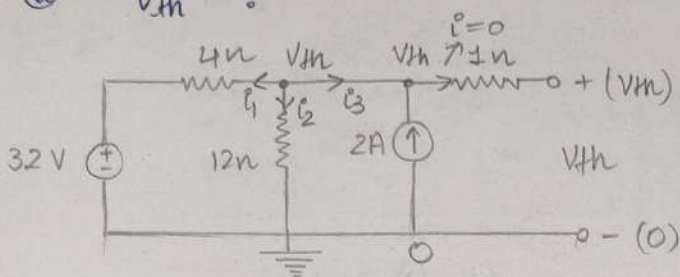


$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_x - 0 - 32}{4} + \frac{V_x - 0}{12} + (-2) = 0$$

$$V_x = 30 \text{ V} \quad (V_x = V_{th})$$


③  $R_{th}$  :-

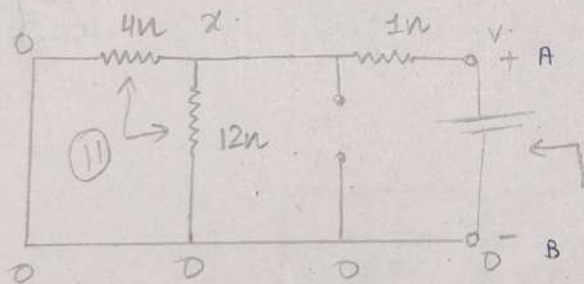

$$\frac{48}{16} = 3$$

$$R_{eq} = 4 \Omega$$

$$R_{th} = 4 \Omega$$

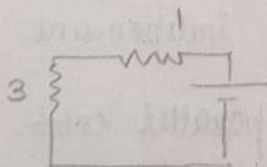

④

Steps :-

- ★ Remove all the independent sources (turning off).
- ★ Calculate  $R_{eq}$  looked from AB.



Imp.

★ Ind. Voltage source turning off  $\rightarrow$  short circuit

★ Ind. current source turning off  $\rightarrow$  open circuit


② Sample Problem <sup>with</sup> dependent sources -:

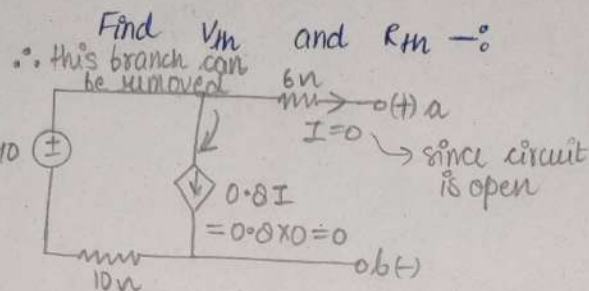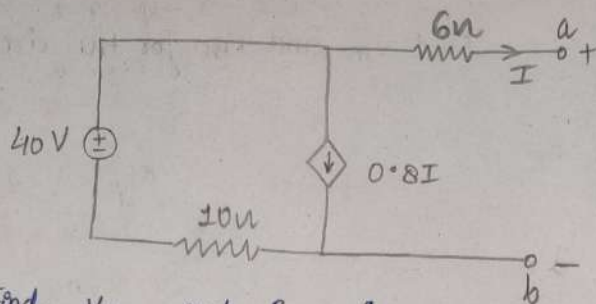★ In this case we can't find out eq. Resistance directly. Hence, we have to take a current or voltage source across a & b, with any value, in this case for simplicity we have taken 1 V.



No current will flow, hence there will be no voltage drop across resistance -

∴  $V_{th} = 40V$

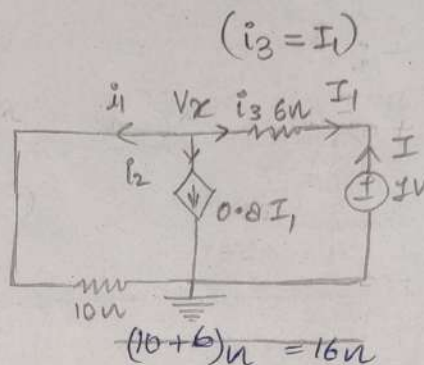

$$\frac{V_x}{10} + 0.8I_1 + I_1 = 0 \quad \left| \quad I_1 = \frac{V_x - 1}{6} \rightarrow (2) \right.$$


$$V_x + 10I_1 = 0 \rightarrow (1)$$

$$V_x = \frac{3}{4} V$$

$$R_{th} = \frac{24}{10} \Omega$$

$$I = I_1$$
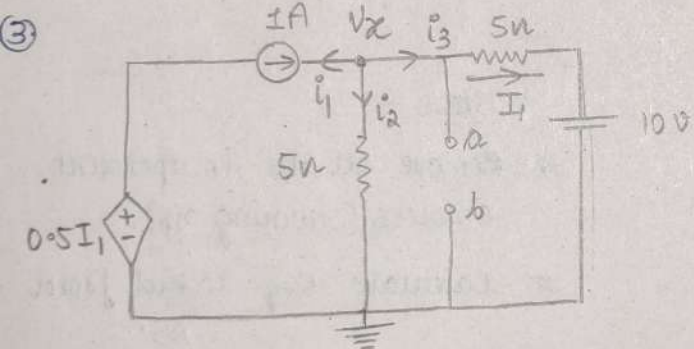
$$I = \frac{1 - V_x}{6} = \frac{1}{24} A$$



Find  $R_{th}$  &  $V_{th}$ .

[GATE ECE 2005]

(i)  $V_x = V_{th}$   $i_1 = -1$


$$i_1 + i_2 + i_3 = 0$$

$$-1 + \frac{V_x}{5} + \frac{V_x - 10}{5} = 0$$

$$2V_x = 15$$

$$V_x = 7.5 V$$

$$V_{th} = 7.5 V$$

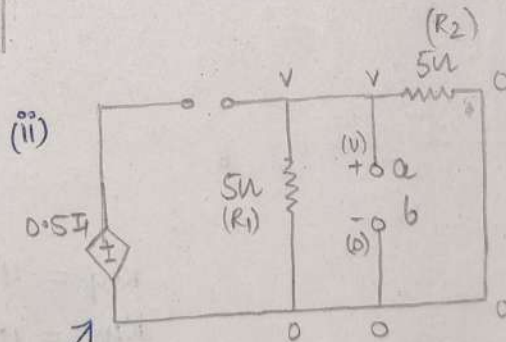

After turning off independent sources

$R_1$  &  $R_2$  are in parallel comb.


$$R_{eq} = \frac{5}{2} = 2.5 \Omega$$

$$R_{th} = 2.5 \Omega$$


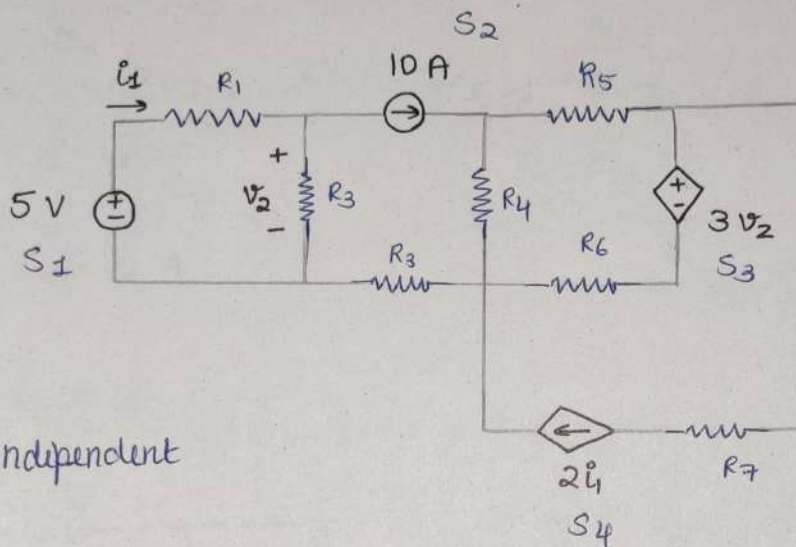
## Dependent and Independent Sources -

- ① Independent source - The element for which both voltage and current don't depend on the voltage or current elsewhere in the circuit.
- ② Dependent source - The element for which either the voltage and current depends on the voltage or current elsewhere in the circuit.



$S_1, S_2 \rightarrow$  Independent

$S_4 \rightarrow$  Dependent upon current in other <sup>part</sup> of circuit.

$S_3 \rightarrow$  Dependent

$$V_x + \frac{18V_x}{6} - \frac{18}{6} = 0$$

$$4V_x - 3 = 0$$


$$V_x = 3/4$$

$$R_{th} = \frac{5}{I} = \frac{5 \times 24}{20A}$$

# Mesh Analysis

Norton  $\rightarrow$  Source Transf.

## Sample Problem (1)

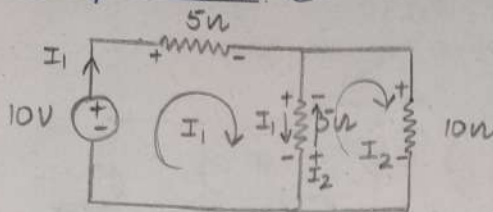

\* Is mesh ke eq. likh kr uss mesh ke current ko guess kr manege.

M<sub>1</sub>

$$10 - 5I_1 - 5(I_1 - I_2) = 0$$

$$2I_1 - I_2 = 0$$


M<sub>2</sub>

$$-5(I_2 - I_1) - 10I_2 = 0$$

$$I_1 - 3I_2 = 0$$

$$I_2 = \frac{2}{5} \text{ A}$$

## Sample Problem (2)

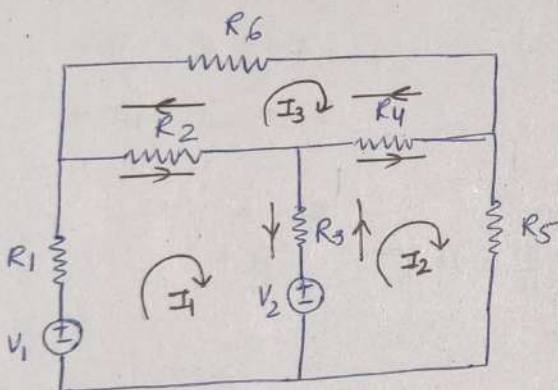

Mesh 1

$$V_1 - I_1 R_1 - R_2(I_1 - I_3) - R_3(I_1 - I_2) - V_2 = 0$$

Mesh 2


$$V_2 - R_3(I_2 - I_1) - R_4(I_2 - I_3) - R_5 I_2 = 0$$

Mesh 3


$$-R_2(I_3 - I_1) - I_3 R_3 - R_4(I_3 - I_2) = 0$$



# Sample Problem ③

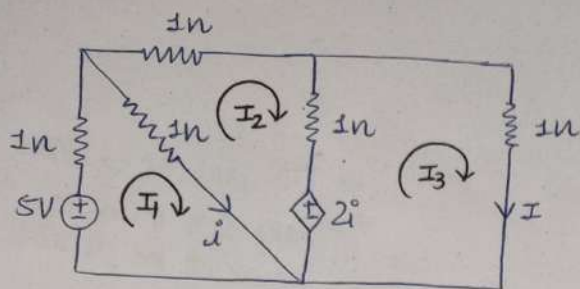

$$I = I_3$$

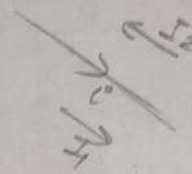

$$I = I_1 - I_2 \rightarrow (4)$$

M1

$$5 - I_1 - (I_1 - I_2) = 0 \rightarrow (1)$$

$$5 - 2I_2 + I_2 = 0 \rightarrow (7)$$

M2

$$-I_2 - (I_2 - I_3) - 2i - (I_2 - I_1) = 0 \rightarrow (2)$$

M3

$$-I_3 + 2i - (I_3 - I_2) = 0 \rightarrow (3)$$

$$-I_2 - I_2 + I_3 - 2I_1 + 2I_2 - I_2 + I_1 = 0$$

$$-I_1 + I_3 - I_2 = 0 \rightarrow (5)$$

$$-I_3 + 2I_1 - 2I_2 - I_3 + I_2 = 0$$


$$2I_3 + 2I_1 - I_2 = 0 \rightarrow (6)$$

$$-2I_3 + 5 = 0$$

$$\boxed{I_3 = \frac{5}{2}}$$



## Mesh Analysis - with current source

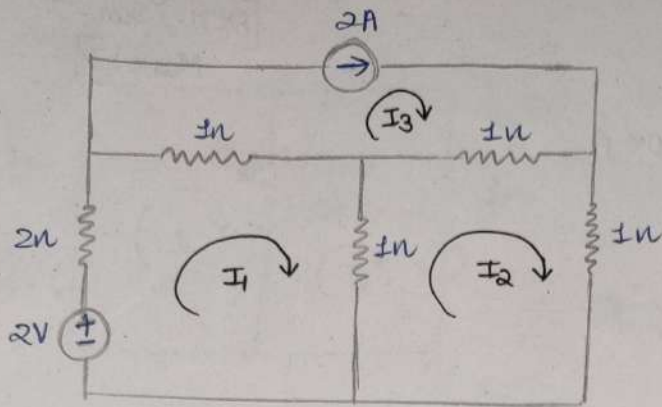

$$I_3 = 2A \rightarrow \textcircled{3}$$

mesh 1

$$2 - 2i_1 - (i_1 - i_3) - (i_1 - i_2) = 0$$

$$-4i_1 + i_2 + i_3 = -2 \rightarrow \textcircled{1}$$

$$-4i_1 + i_2 = -4$$

$$-12i_1 + 3i_2 = -12$$

$$-11i_1 = -14$$

$$i_1 = \frac{14}{11}$$

$$i_2 = \frac{12}{11}$$


mesh 2

$$-(i_2 - i_1) - (i_2 - i_3) - i_2 = 0$$

$$i_1 - 3i_2 + i_3 = 0 \rightarrow \textcircled{2}$$

$$-i_1 + 3i_2 = 2$$

# Sample Problem

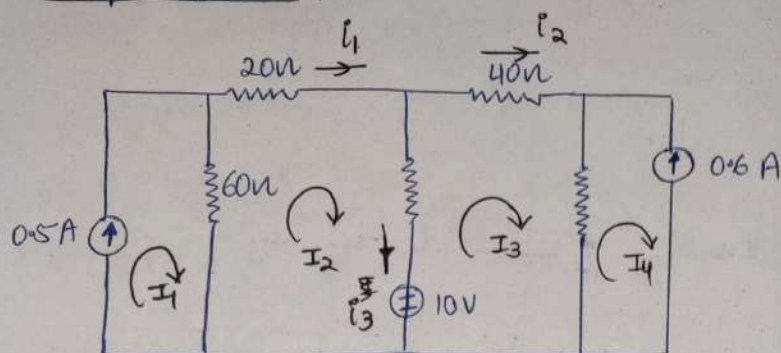

[AKTU Sem-I  
Marks: 7]

$$I_1 = 0.5A$$

$$I_4 = -0.6A$$

mesh ②

$$-60(I_2 - I_1) - 20I_2 - 15(I_2 - I_3) - 10 = 0$$

$$-60I_2 + 60I_1 - 20I_2 - 15I_2 + 15I_3 - 10 = 0$$

$$-95I_2 + 60I_1 + 15I_3 - 10 = 0$$

$$-95I_2 + 15I_3 + 20 = 0$$

$$19I_2 - 3I_3 + 4 = 0 \rightarrow \text{①}$$

mesh ③

$$10 - 15(I_3 - I_2) - 40I_3 - 100(I_3 - I_4) = 0$$

$$10 - 15I_3 + 15I_2 - 40I_3 - 100I_3 + 100I_4 = 0$$

$$-155I_3 + 15I_2 - 70 = 0$$

$$-31I_3 + 3I_2 - 14 = 0 \rightarrow \text{②}$$

$$I_2 = \quad \quad I_3 = \quad$$

$$i_1 = I_2$$


$$i_3 = I_2 - I_3$$

$$i_2 = I_3$$




# Supermesh Analysis

Sample ①

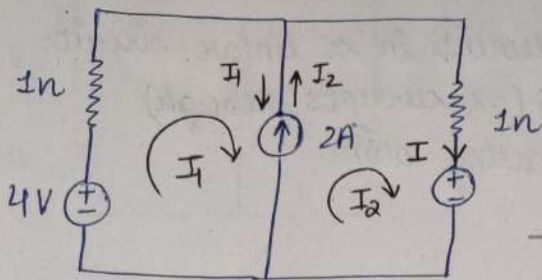

Find  $I$

super mesh

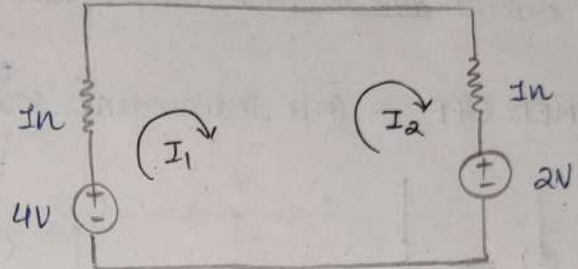

$$I_2 - I_1 = 2 \rightarrow \textcircled{2}$$

Add ① + ②

$$I_2 = I = 2A$$


$$4 - I_1 - I_2 - 2 = 0$$

$$I_1 + I_2 = 2 \rightarrow \textcircled{1}$$

Sample ②

Find Power delivered by  $V_1$ .

[GATE 2010]

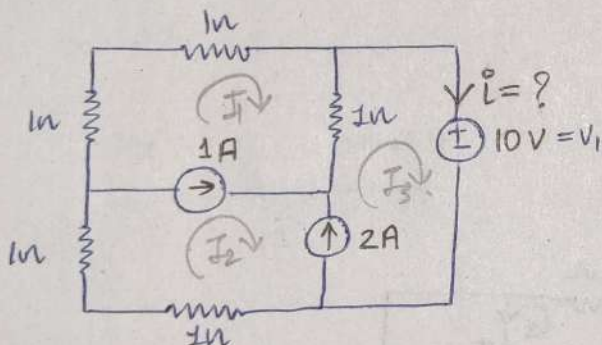

$$I_2 - I_1 = 1A \rightarrow \textcircled{2}$$

$$I_3 - I_2 = 2A \rightarrow \textcircled{3}$$


$$-I_1 - I_2 - 10 - 2I_2 = 0$$

$$I_1 + I_2 = -5 \rightarrow \textcircled{1}$$

$$I_2 = -2$$

Therefore  $I_3 = 0$

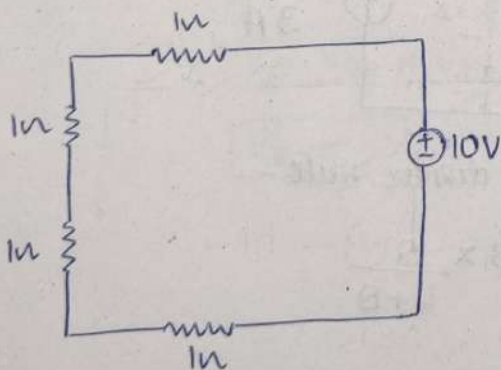
Power delivered by voltage source  
source = 0 W




## Superposition Theorem -

The voltage across (or current through) on element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

TURNED OFF - (All independent sources)

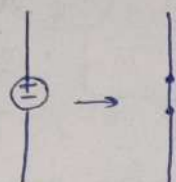

Voltage source



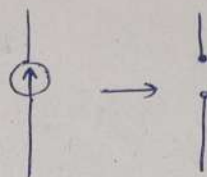


Current source

\* The dependent sources are left as it is.

### Sample Problem (I)


Find 'V' by Superposition Theorem

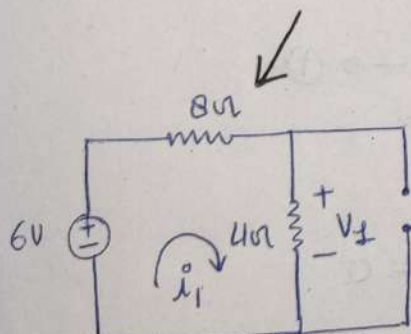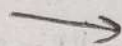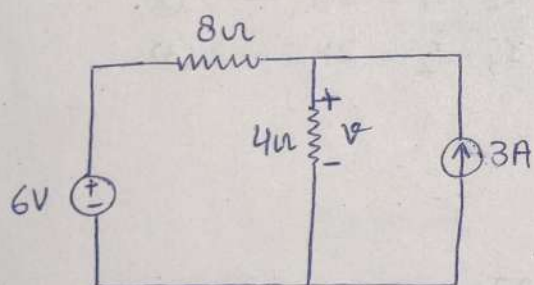

$$i_1 = \frac{6}{8+4}$$

$$i_1 = 0.5 \text{ A}$$

$$V_1 = 0.5 \times 4 = 2 \text{ V}$$

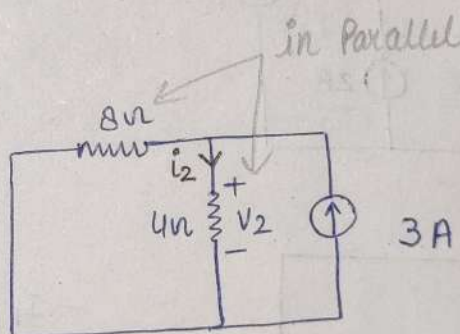

By current divider rule -

$$i_2 = 3 \times \frac{8}{4+8}$$

$$i_2 = 2 \text{ A}$$



$$V_2 = 2 \times 4 = 8 \text{ V}$$

$$V = V_1 + V_2$$

$$V = 10 \text{ V}$$


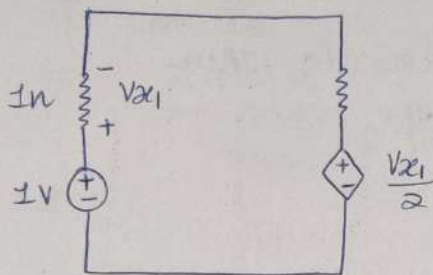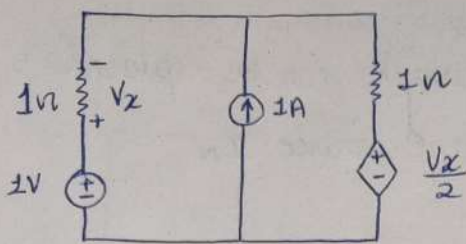
# Sample Problem - (2) [with Dependent sources]




$$1 - 2i - \frac{V_{x1}}{2} = 0 \quad \left( i = \frac{V_{x1}}{1} \right)$$

$$1 - 2V_{x1} - \frac{V_{x1}}{2} = 0$$

$$V_{x1} = \frac{2}{5} = 0.4 \text{ V}$$

$$V_x = V_{x1} + V_{x2}$$

$$V_x = 0$$

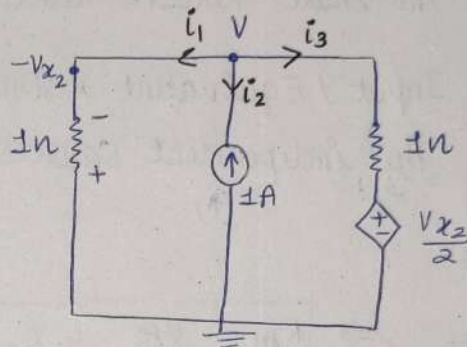

$$V = -V_{x2}$$

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V}{1} + (-1) + \frac{V - \frac{V_{x2}}{2}}{1} = 0$$

$$-V_{x2} - V_{x2} - \frac{V_{x2}}{2} = 1$$

$$V_{x2} = -\frac{2}{5}$$

## NORTON'S THEOREM -:

A linear and bi-directional two-terminal network can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ .



$I_N \rightarrow$  The short-circuit current through the terminals.

$R_N \rightarrow$  Input / Equivalent resistance at the terminals when the independent sources are turned off.

$$R_N = R_{th}$$

$$I_N = \frac{V_{th}}{R_{th}} \Rightarrow R_{th} = \frac{V_{th}}{I_N} = R_N$$


Source transformation.

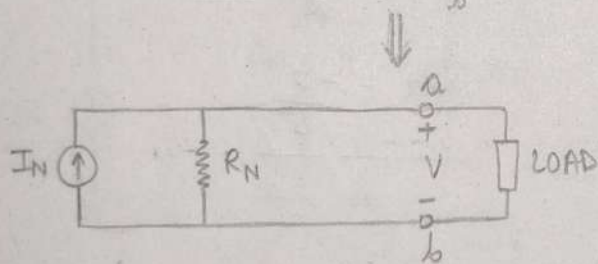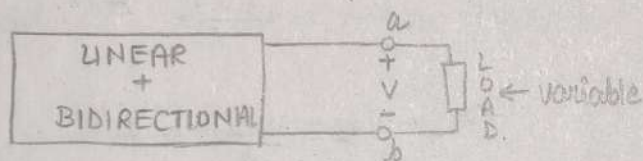



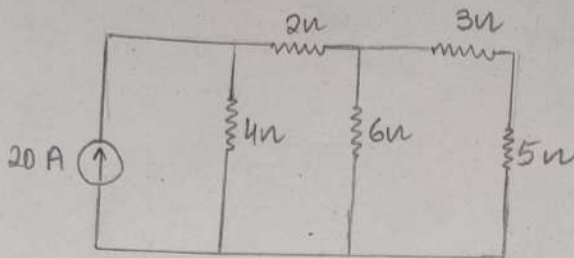
# Sample Problem (1)

Find the current flowing through 5Ω resistor.



To find  $I_N$  —:

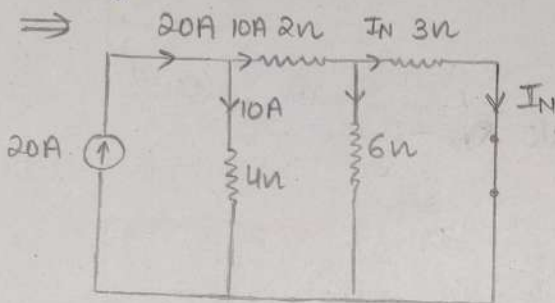

$$I_N = 10 \times \frac{6}{6+3} \quad \left. \vphantom{I_N = 10 \times \frac{6}{6+3}} \right\} \text{By current divider rule}$$


$$I_N = \frac{20}{3} \text{ A}$$

$$(3 \parallel 6) \Omega \rightarrow 11$$




$$R_{eq} = 2 \Omega$$

$$2 \Omega \parallel 2 \Omega \rightarrow \text{series}$$


$$R_{eq} = 4 \Omega$$

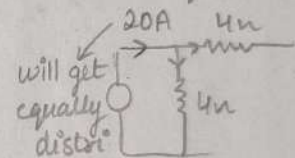

To find  $R_N$  —:

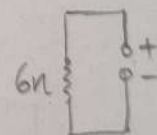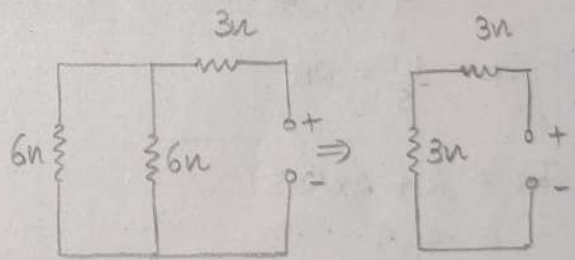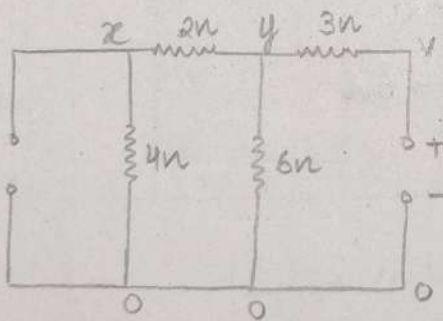

$$R_N = 6 \Omega$$

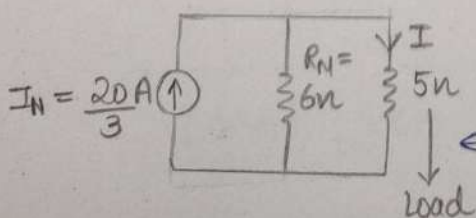


Norton's eq. circuit

$$I = \frac{20}{3} \times \frac{6}{6+5}$$


$$I = \frac{40}{11}$$

Sample Problem 2  $\rightarrow$  (with Dependent source)

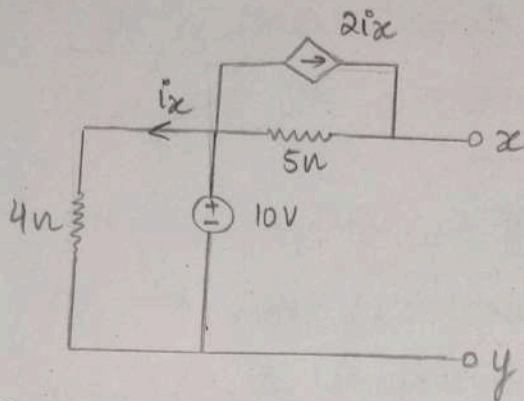Develop the Norton's equivalent circuit between the terminals  $x$  and  $y$ .



(i) calculate  $I_N$  -:

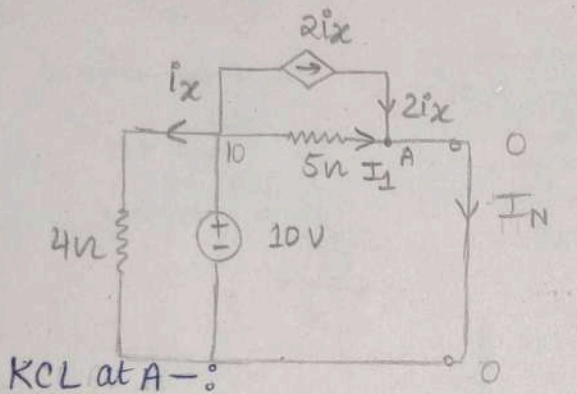


$$I_N = I_1 + 2i_x \rightarrow \text{---} \text{---}$$

$$i_x = \frac{10}{4} = \frac{5}{2} = 2.5 \text{ A}$$

$$I_1 = \frac{10}{5} = 2 \text{ A}$$

$$I_N = 2 + 2 \times (2.5) = 7 \text{ A}$$


(ii) calculate  $R_N$  -:

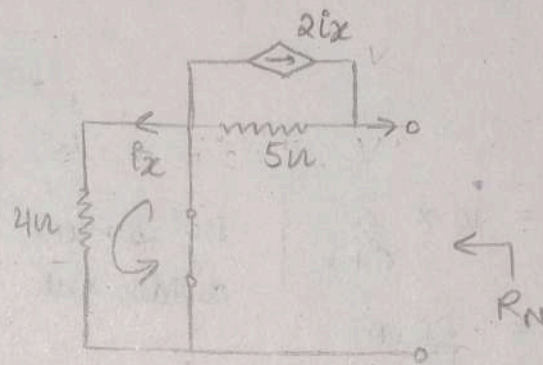

$$i_x = 0 \text{ A}$$

$$2i_x = 0$$

$$\therefore R_N = 5 \Omega$$

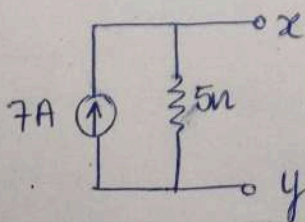

Norton's equ circuit







# SOURCE TRANSFORMATION


$$R_{Th} = R_N = \frac{V_{Th}}{I_N}$$

$$T \longleftrightarrow N$$

$$VS \longleftrightarrow CS$$

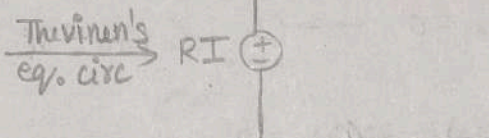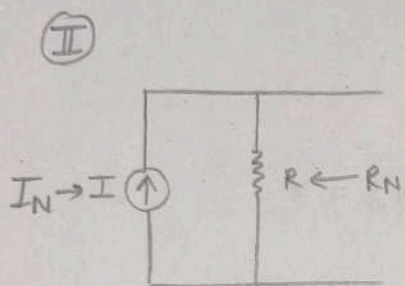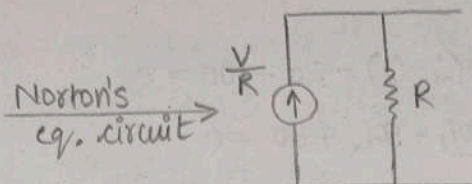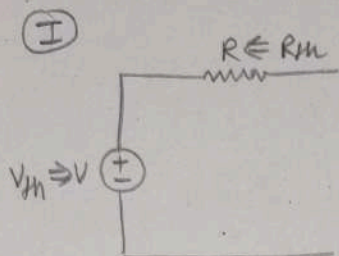


## Example

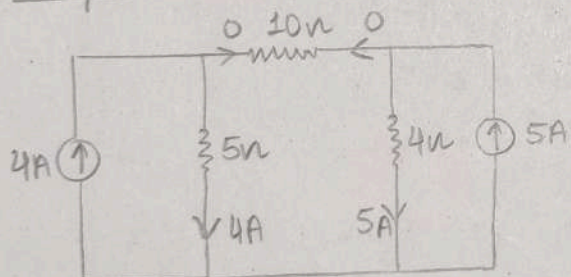

⇒ currents in branches are given


↓ By source transformation

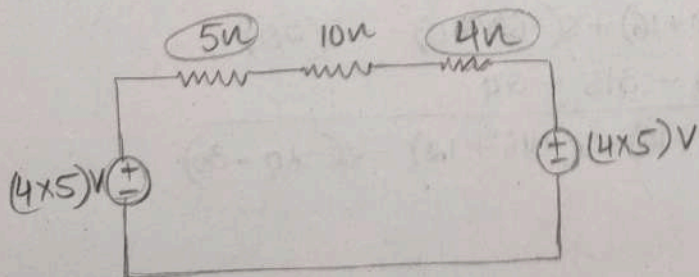

Do not perform calculation for transformed resistors.



Ques)  
Mesh  
Analysis

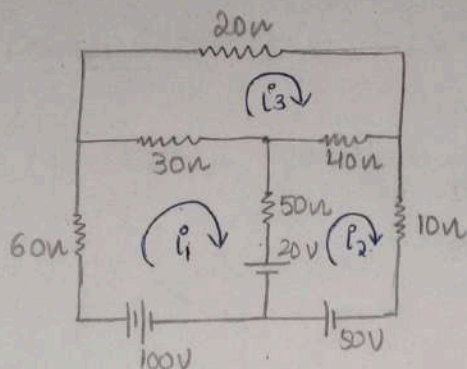

$$-60i_1 - 30(i_1 - i_3) - 50(i_1 - i_2) - 20 + 100 = 0$$

$$-60i_1 - 30i_1 + 30i_3 - 50i_1 + 50i_2 + 80 = 0$$

$$+14i_1 - 3i_3 - 5i_2 = 80 \rightarrow (1)$$

$$20 - 50(i_2 - i_1) - 40(i_2 - i_3) - 10i_2 + 50 = 0$$

$$70 - 50i_2 + 50i_1 - 40i_2 + 40i_3 - 10i_2 = 0$$

$$70 - 10i_2 + 50i_1 + 40i_3 = 0 \rightarrow (2) \quad 10i_2 - 5i_1 - 4i_3 = 7$$

$$-30(i_3 - i_1) - 40(i_3 - i_2) - 20(i_3) = 0$$

$$-30i_3 + 30i_1 - 40i_3 + 40i_2 - 20i_3 = 0$$

$$-90i_3 + 30i_1 + 40i_2 = 0 \rightarrow (3)$$

$$\begin{bmatrix} 14 & -5 & -3 \\ -5 & 10 & -4 \\ 3 & 4 & -9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 80 \\ 7 \\ 0 \end{bmatrix}$$

$$i_1 = \frac{D_{x1}}{D}$$


$$i_1 = \frac{\begin{vmatrix} 8 & -5 & -3 \\ 7 & 10 & -4 \\ 0 & 4 & -9 \end{vmatrix}}{\begin{vmatrix} 14 & -5 & -3 \\ -5 & 10 & -4 \\ 3 & 4 & -9 \end{vmatrix}} = \frac{8(-90+16) + 5(-63+0) - 3(20)}{14(-90+16) + 5(+45+12) - 3(-20-30)}$$

Similarly —  $= 1.65A$


$$i_2 = 2.12A \quad \& \quad i_3 = 1.5A$$




Plus)  
SPT

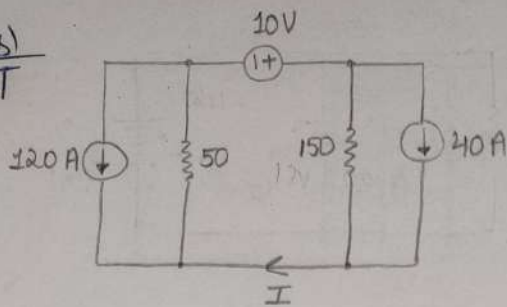

calculate current load I

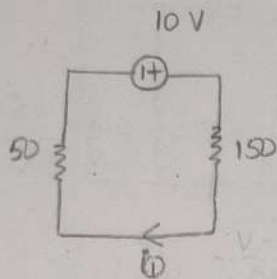

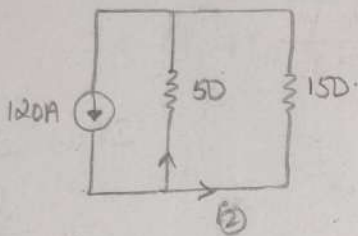
$$i_1 = \frac{10}{200} = 0.05 \text{ A}$$



$$i_2 = \left( \frac{50}{50+150} \right) \times 120 \quad (\text{By current divider rule})$$

$$= \frac{120}{4} = 30 \text{ A}$$

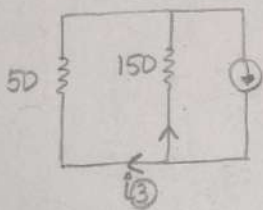


$$i_3 = \left( \frac{150}{50+150} \right) \times 40$$

$$i_3 = \frac{3}{4} \times 40 = 30 \text{ A}$$

$$i_1 + i_3 - i_2 = 0.05 + 30 - 30$$

$$= 0.05 \text{ A}$$

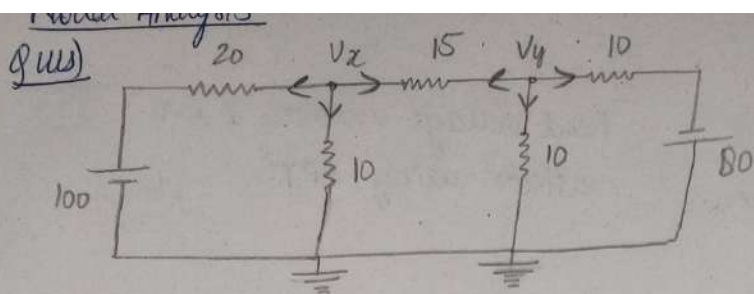

$$\frac{V_x - 100}{20} + \frac{V_x}{10} + \frac{V_x - V_y}{15} = 0$$

$$\frac{V_y - V_x}{15} + \frac{V_y}{10} + \frac{V_y + 80}{10} = 0$$

$$\Rightarrow 2V_y - 2V_x + 3V_y + 3V_y + 240 = 0$$

$$8V_y - 2V_x + 240 = 0$$

$$4V_y - V_x + 120 = 0$$

$$\Rightarrow 3V_x - 300 - 6V_x + 4V_x - 4V_y = 0$$

$$13V_x - 4V_y = 300$$

$$13(4V_y + 120) - 4V_y = 300$$

$$52V_y + 1560 - 4V_y = 300$$

$$48V_y = -1260$$

$$V_y = \frac{-1260}{48} = -26.25$$

$$V_{x0} = 15V$$


$$V_x - V_y / 15$$

$$i = \frac{(+26.25) + (15)}{15} = 2.75$$


$\Rightarrow$  assumed that current through 15Ω flows from  $V_x$   $\therefore$  which comes out to be true.



Ques)  
MA

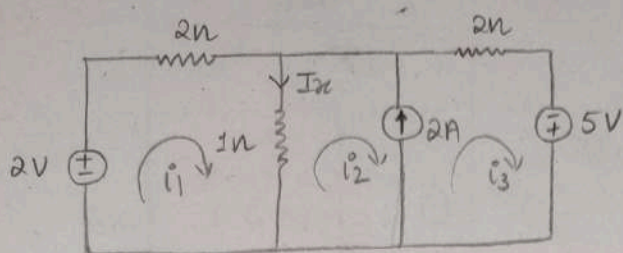

Find  $I_x$

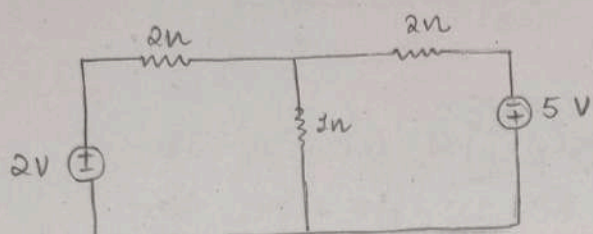

$$i_3 - i_2 = 2$$

$$2 - 3i_1 - 1(i_1 - i_2) = 0$$

$$2 - 3i_1 - i_1 + i_2 = 0$$

$$2 - 4i_1 + i_2 = 0$$

$$-i_2 + i_1 - 2i_3 + 5 = 0$$

$$-i_2 + i_1 - 2(2 + i_2) + 5 = 0$$

$$-i_2 + i_1 - 4 - 2i_2 + 5 = 0$$

$$-3i_2 + i_1 + 1 = 0$$

$$i_2 = \frac{i_1}{3} + \frac{1}{3}$$

$$+2 - 4i_1 + \frac{i_1}{3} + \frac{1}{3} = 0$$

$$\frac{7}{3} = \frac{11i_1}{3}$$

$$i_1 = \frac{7}{11} \text{ A}$$

$$i_2 = \frac{7}{33} + \frac{1}{3}$$

$$i_2 = \frac{10}{33} \text{ A}$$

$$I_x = i_1 - i_2$$


$$= \frac{7}{11} - \frac{10}{33}$$

$$= \frac{3}{33}$$


$$= \frac{1}{11} \text{ A}$$

Ques)

Superposition  
theorem

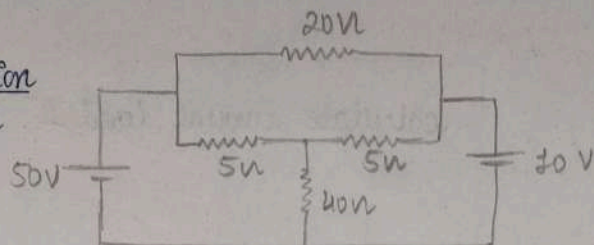

→ current 40Ω  
branch.

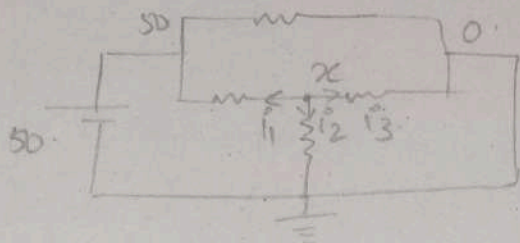

$$\frac{V_x}{40} + \frac{8(V_x - 50)}{5} + \frac{0V_x}{5} = 0$$

$$V_x + 8V_x - 400 + 8V_x = 0$$

$$17V_x = 400$$

$$V_x = \frac{400}{17}$$

$$i_1 = \frac{400 \cdot 10}{17 \times 40}$$

$$\frac{V_x}{40} + \frac{8(V_x - 10)}{5} + \frac{0(V_x)}{5} = 0 \quad i_2 = \frac{0 \cdot 10}{17 \times 40}$$

$$17V_x = 80$$

$$V_x = \frac{80}{17}$$

$$\left( \frac{12}{17} \right)$$


$$V_x = \frac{480}{17}$$

12


$$I = \frac{480}{17 \times 40} = 0.705$$



Ques)  
SPT

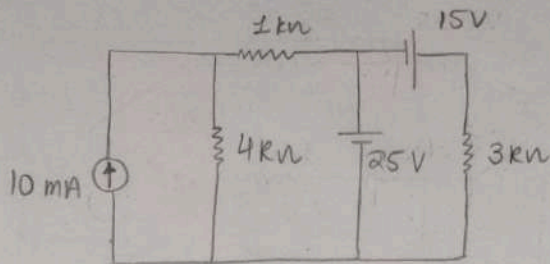


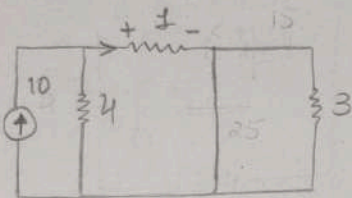Find voltage across  $1\text{ k}\Omega$  resistor using SPT.




$$I = 10 \times \frac{4}{4+1} \quad (\text{By current divider rule})$$

$$I_1 = 8\text{ mA}$$

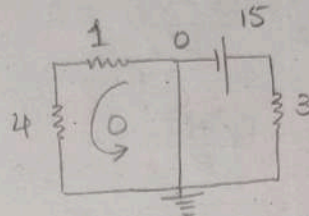

$I$  across  $1\text{ k}\Omega$  resistor  $= 0$

$$I_2 = 0$$

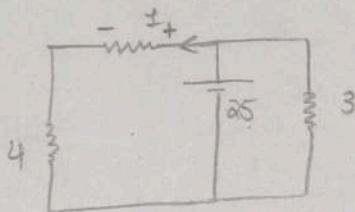

$$V = \frac{1 \times 25}{4+1} \quad (\text{By voltage divider rule})$$

$$V = 5$$

$$I_2 = 5\text{ mA}$$

Since direction of current  $I_1$  &  $I_2$  are different

$$I = (8-5)\text{ mA}$$

$$I = 3\text{ mA}$$

$$V = R \times I$$

$$V = 1\text{ k}\Omega \times 3\text{ mA}$$

$$V = 3\text{ V}$$